



Chapter 4


The Processor

Dr.Randa Mohamed


Agenda

- Single cycle MIPS:
 - Control
 - Datapath (J type)
 - Performance

Full Datapath

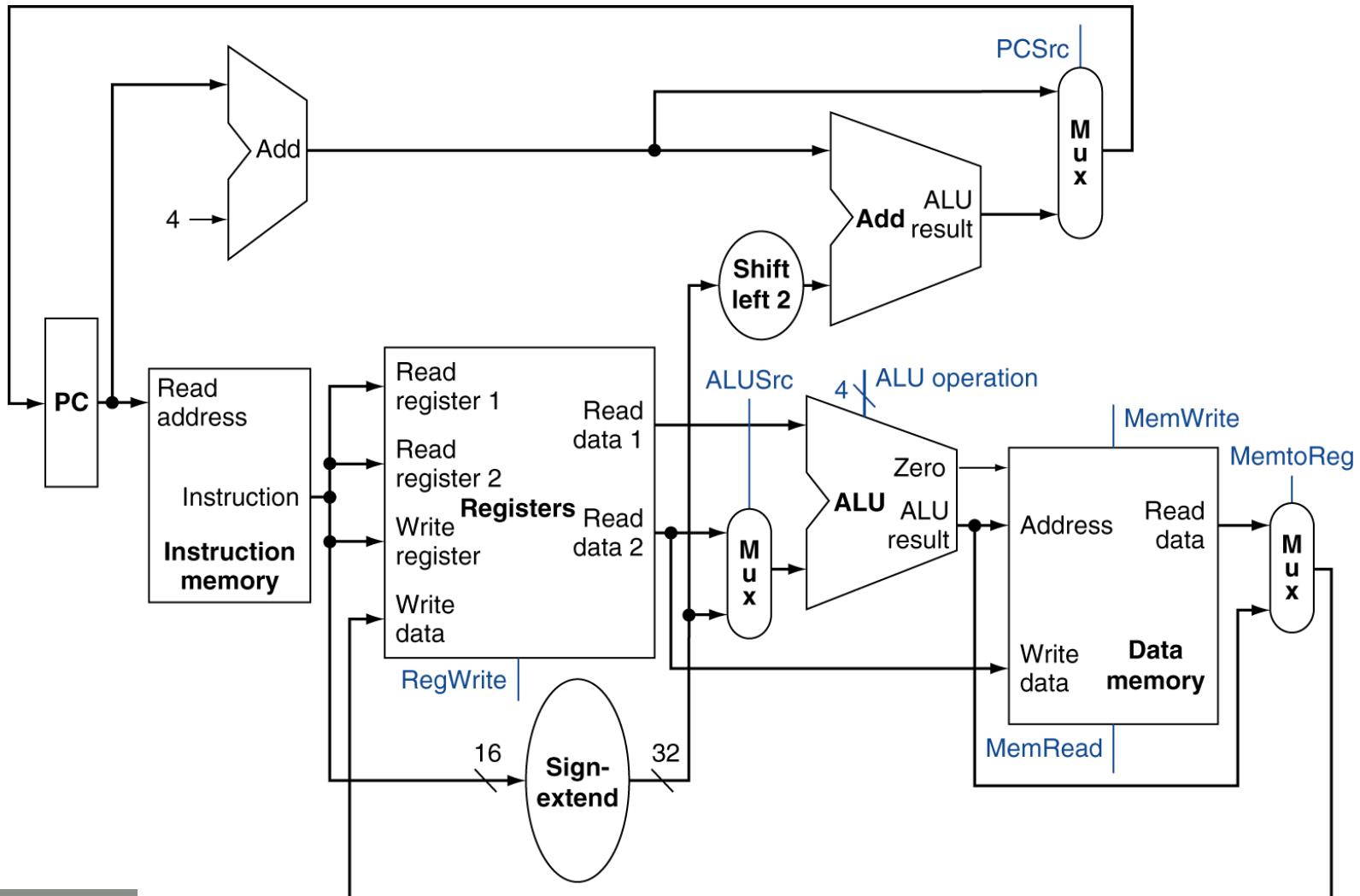


Control

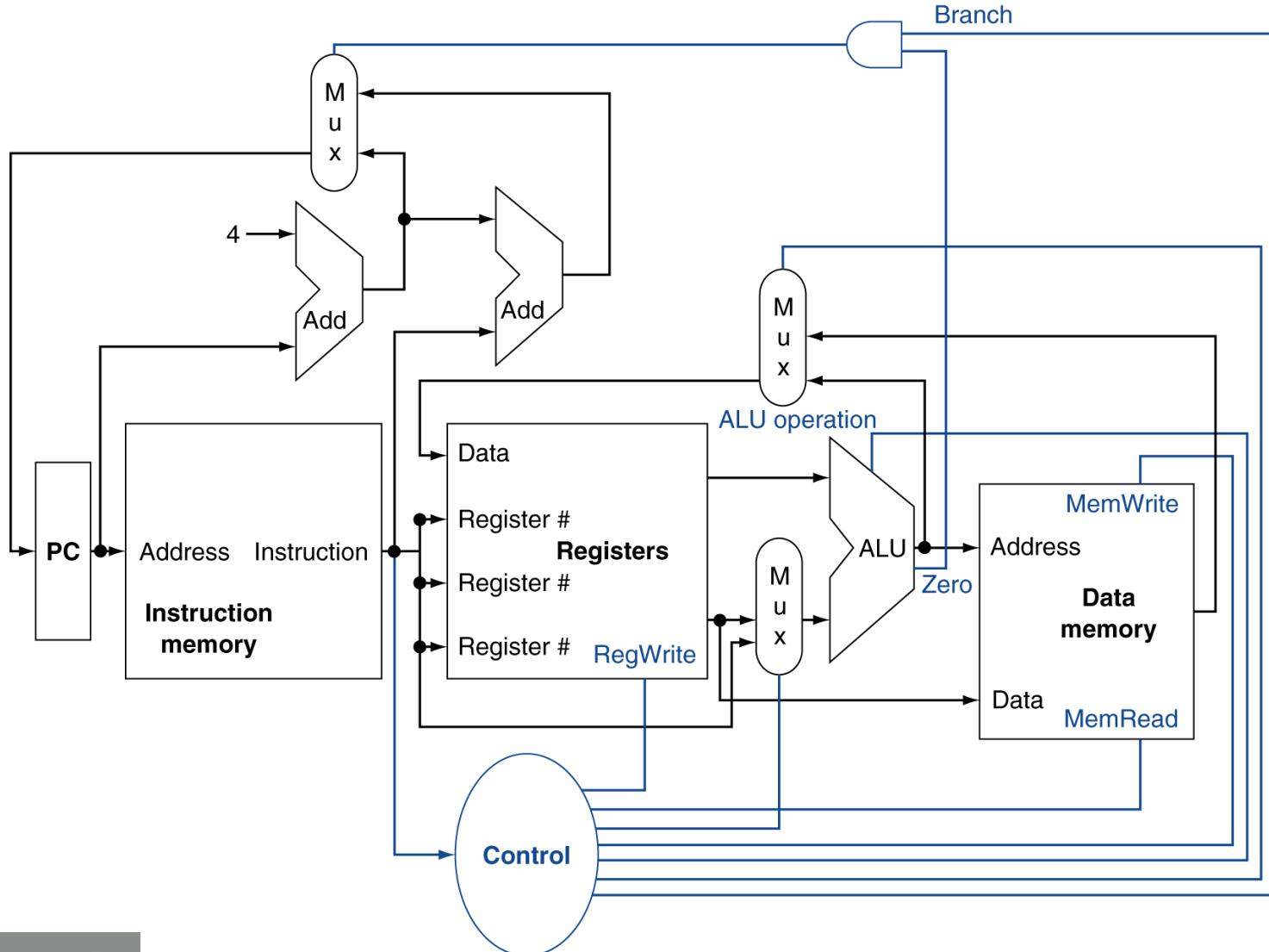


Field bit positions

R-type
I-type

31-26	25-21	20-16	15-11	10-6	5-0
op	rs	rt	rd	shamt	funct
op	rs	rt	16-bit immediate/address		

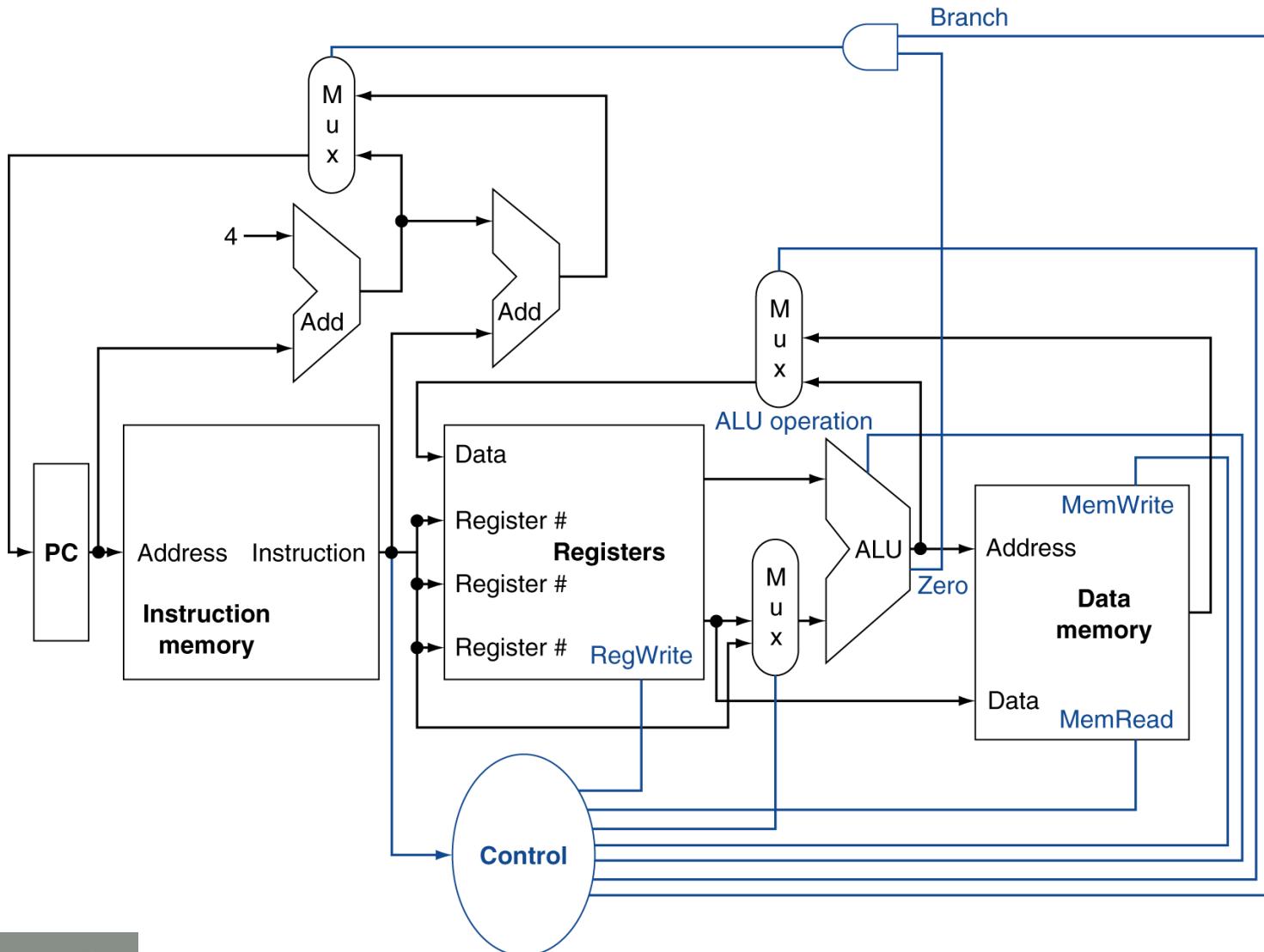

Datapath With Control

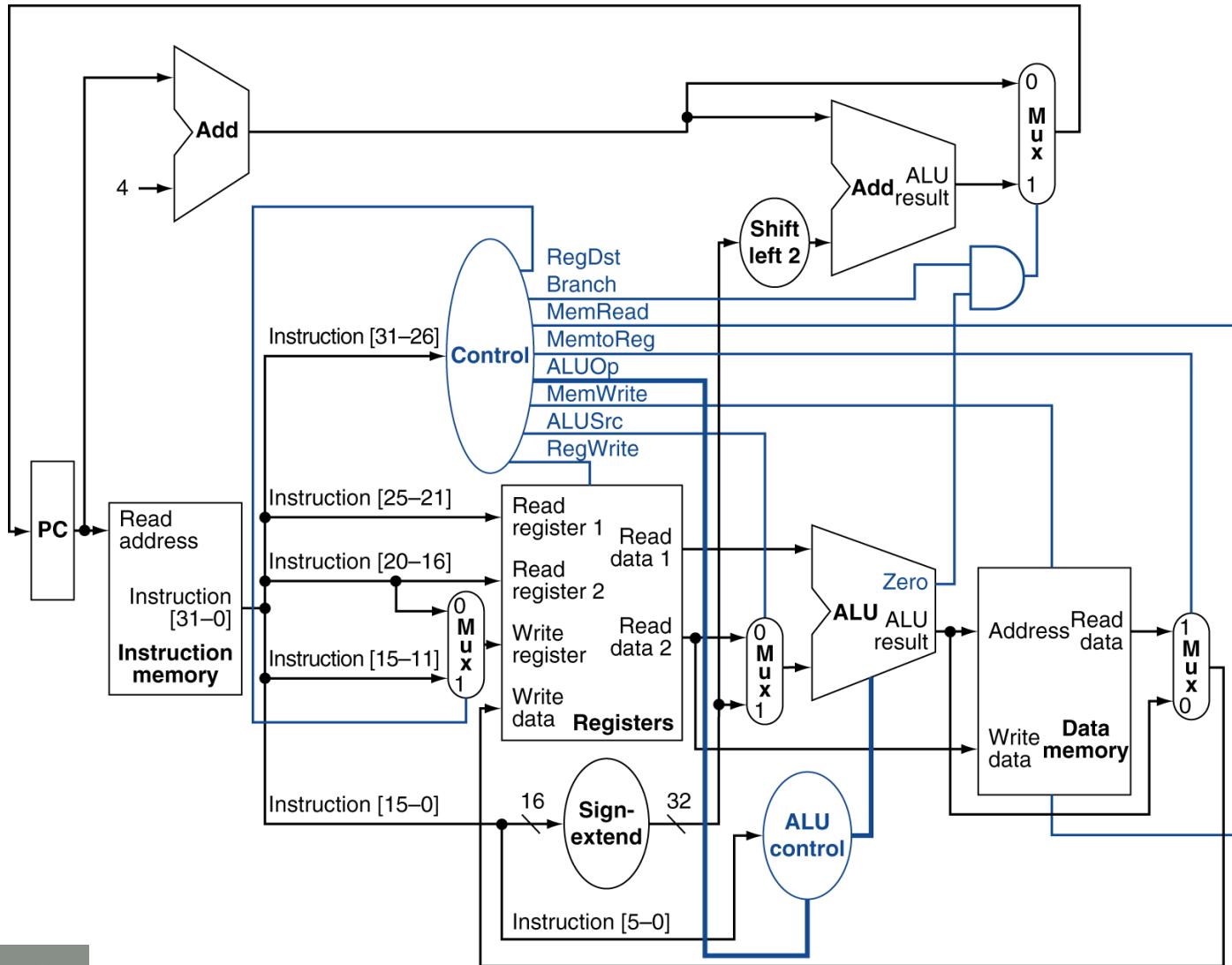

ALU Control

- ALU used for
 - Load/Store: F = add
 - Branch: F = subtract
 - R-type: F depends on funct field

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

ALU Control

- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111


ALU Control

- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

ALUOp		Funct field							Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0		
0	0	X	X	X	X	X	X	0010	
X	1	X	X	X	X	X	X	0110	
1	X	X	X	0	0	0	0	0010	
1	X	X	X	0	0	1	0	0110	
1	X	X	X	0	1	0	0	0000	
1	X	X	X	0	1	0	1	0001	
1	X	X	X	1	0	1	0	0111	

ALU Control

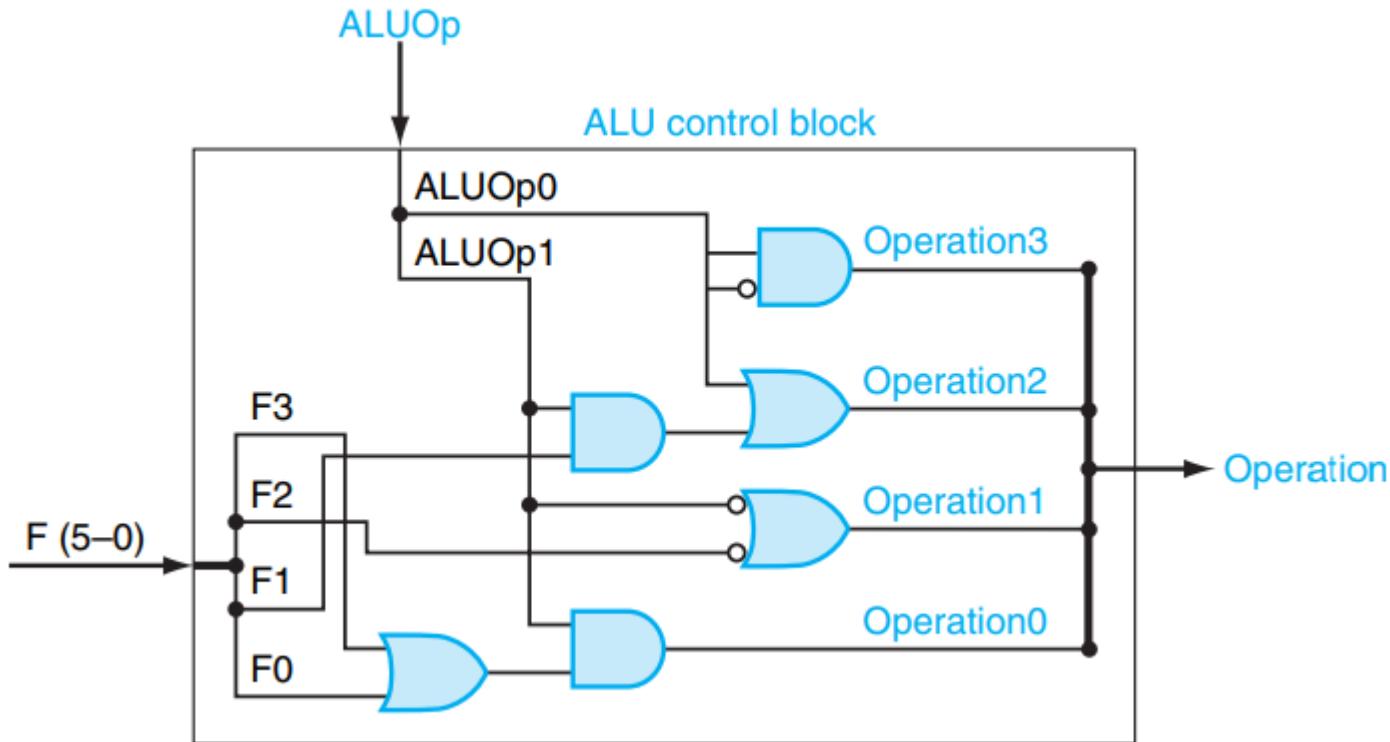
- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control




ALU Control

- Assume 2-bit ALUOp derived from opcode

ALUOp		Funct field							Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0		
0	0	X	X	X	X	X	X	0010	
X	1	X	X	X	X	X	X	0110	
1	X	X	X	0	0	0	0	0010	
1	X	X	X	0	0	1	0	0110	
1	X	X	X	0	1	0	0	0000	
1	X	X	X	0	1	0	1	0001	
1	X	X	X	1	0	1	0	0111	

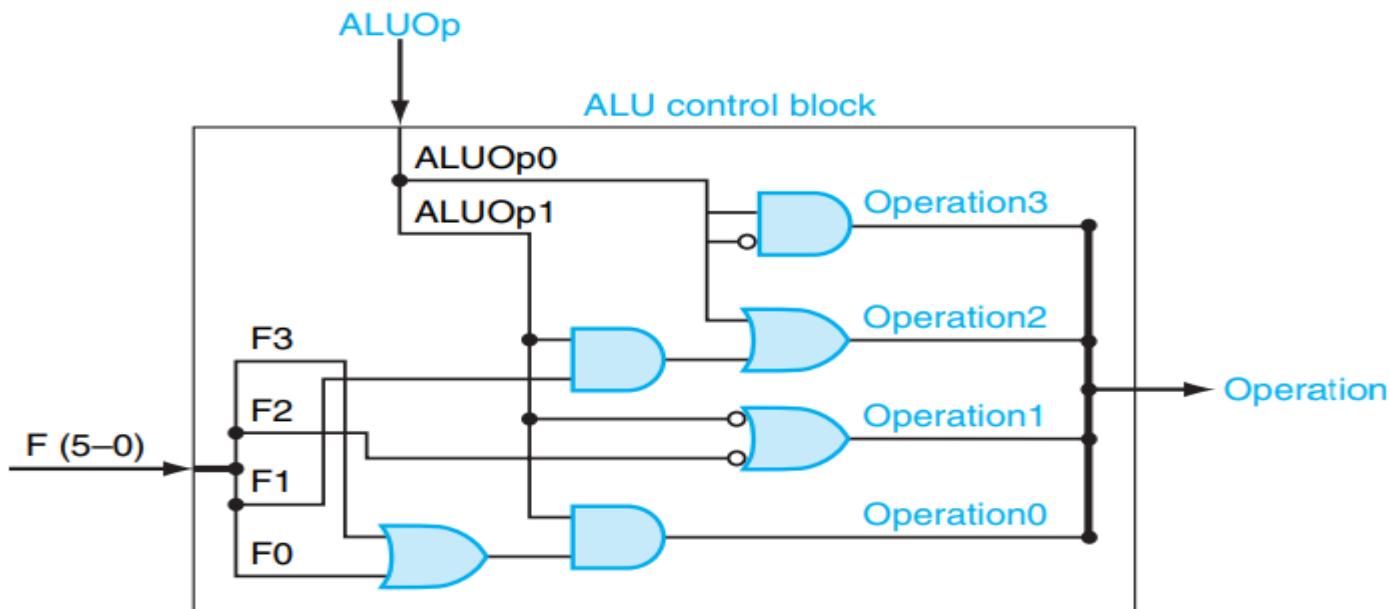


Datapath With Control

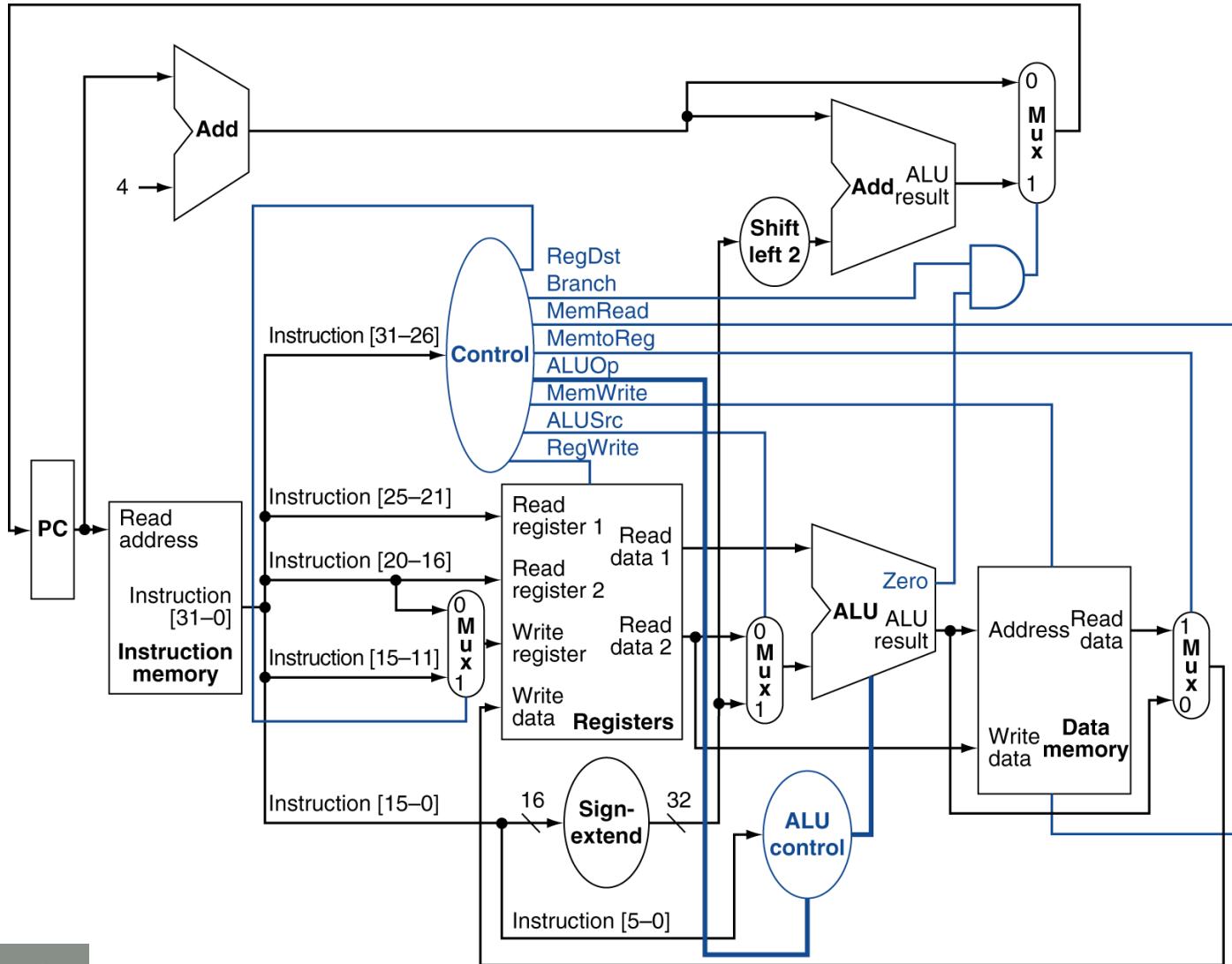

The Main Control Unit

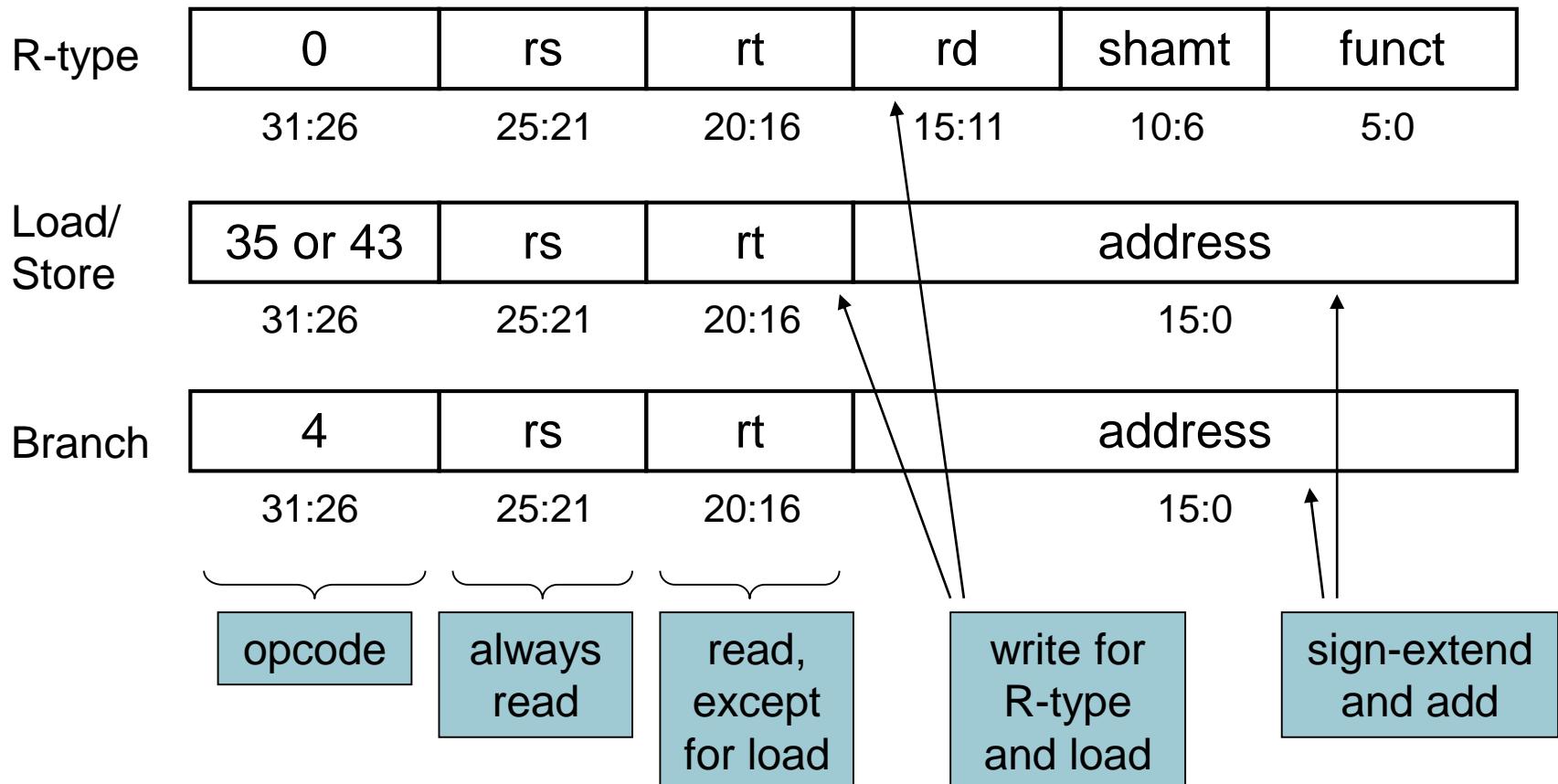- Control signals derived from instruction



The Main Control Unit


- Control signals derived from instruction

Control	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1


R-format	000000
Lw	100011
sw	101011
beq	000100

The Main Control Unit

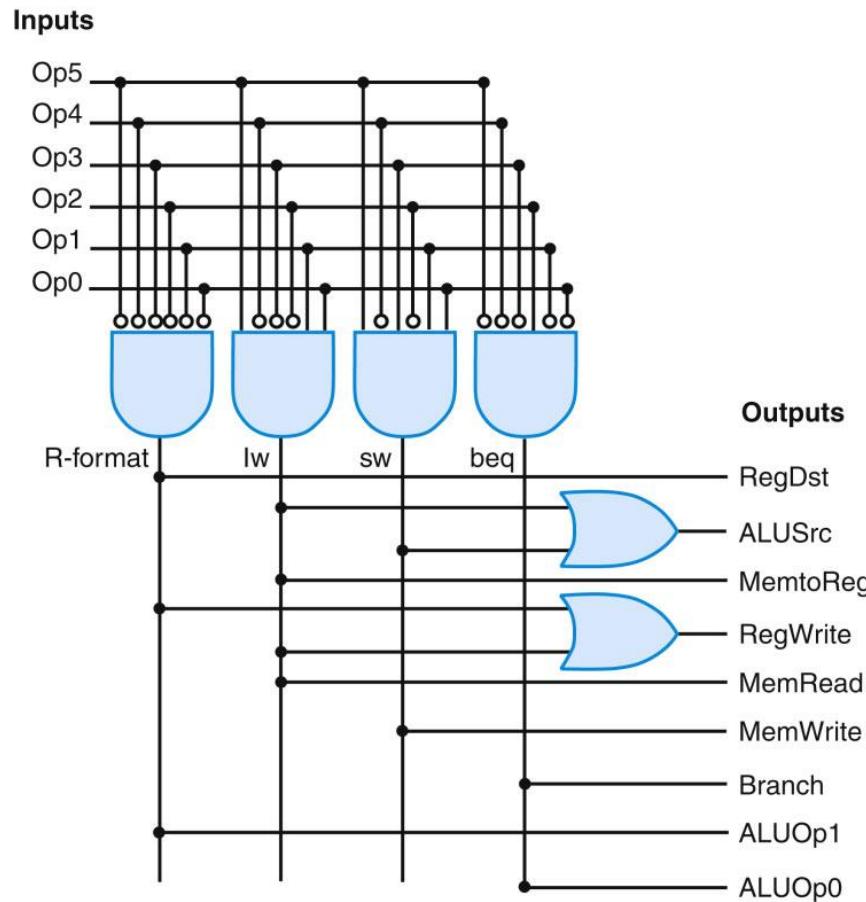
- Control signals derived from instruction




R-Type Instruction

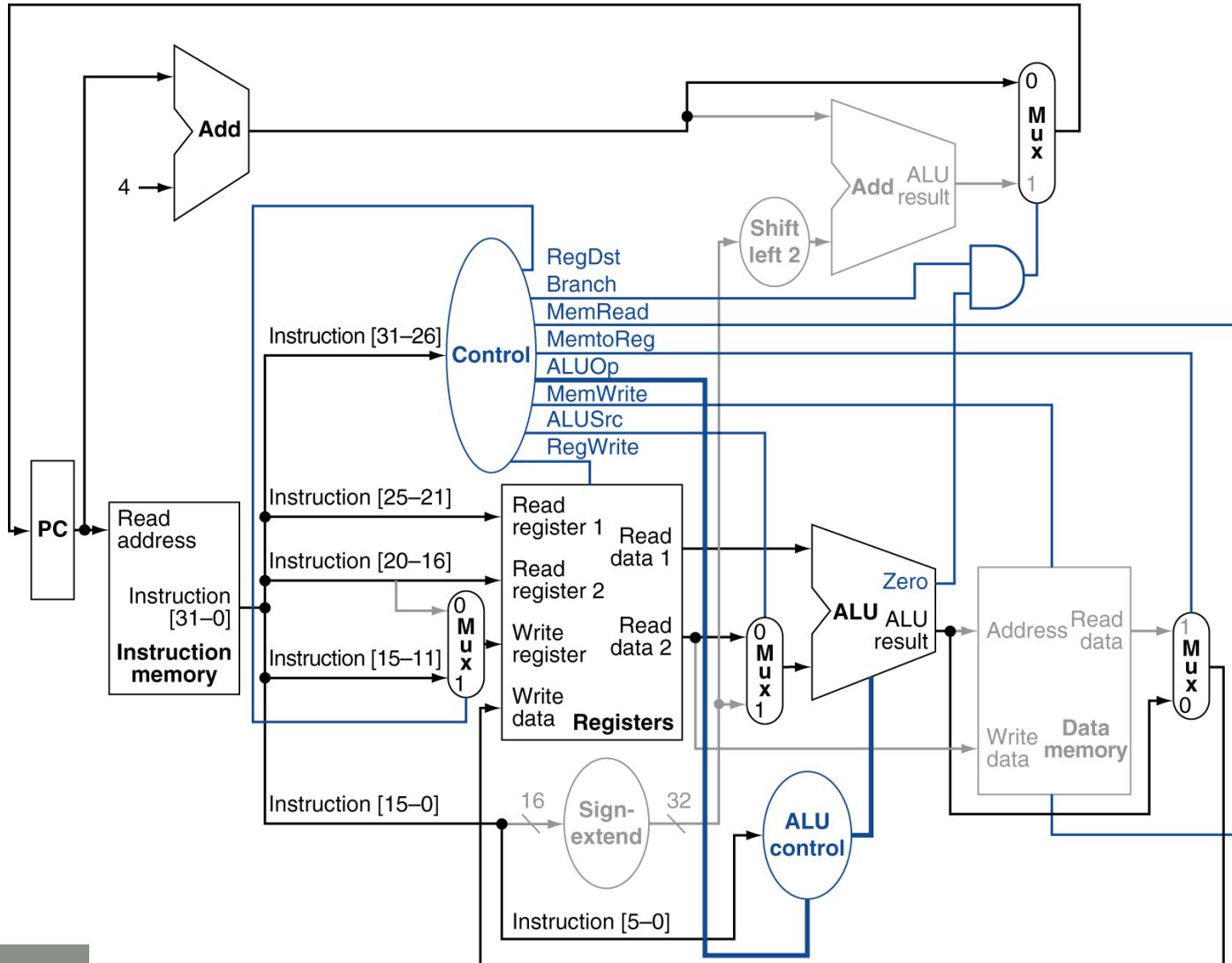

Load Instruction

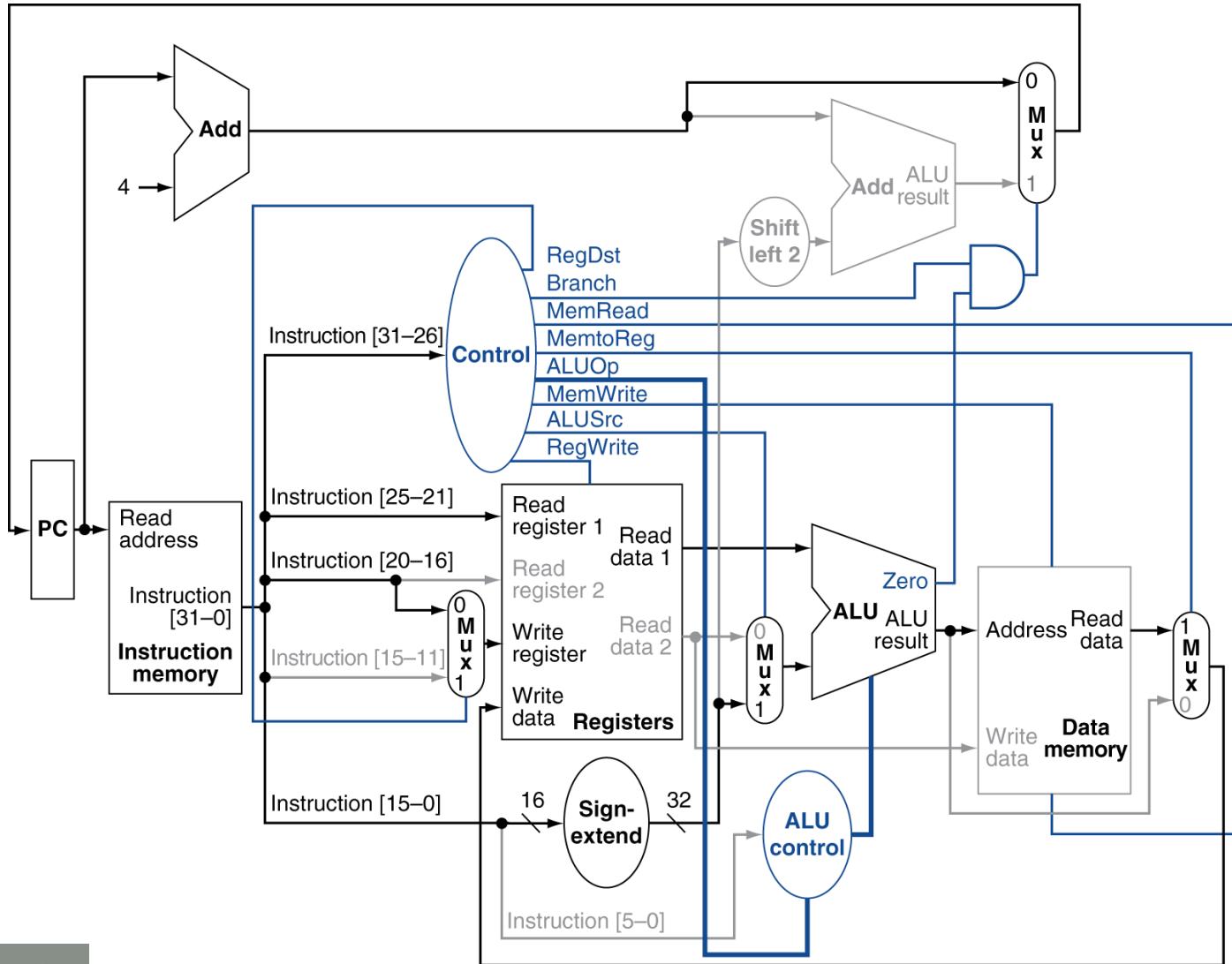

Branch-on-Equal Instruction

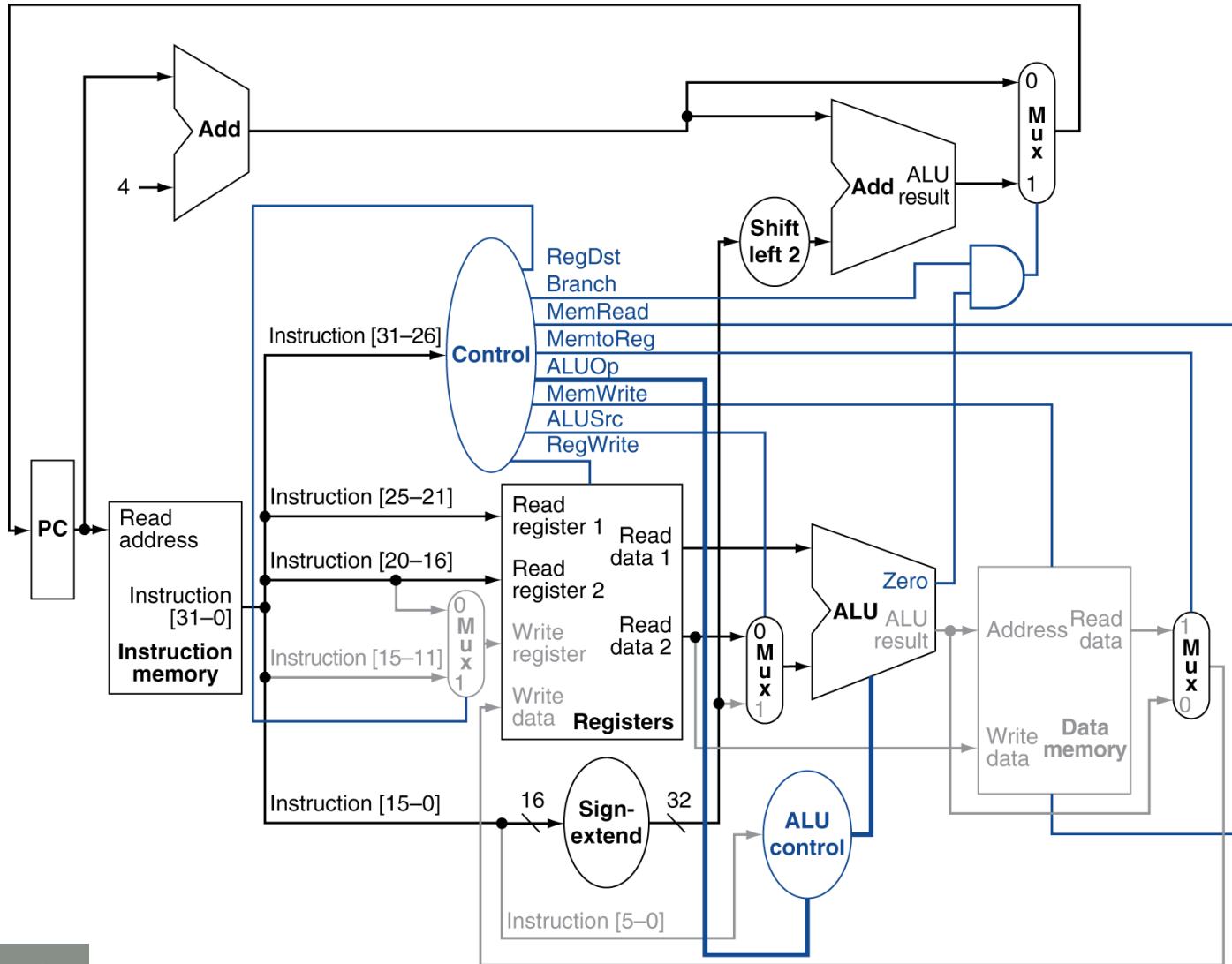

Implementing Jumps

Jump

2


address

31:26

25:0

- Jump uses word address
- Update PC with concatenation of
 - Top 4 bits of old PC
 - 26-bit jump address
 - 00
- Need an extra control signal decoded from opcode

Datapath With Jumps Added

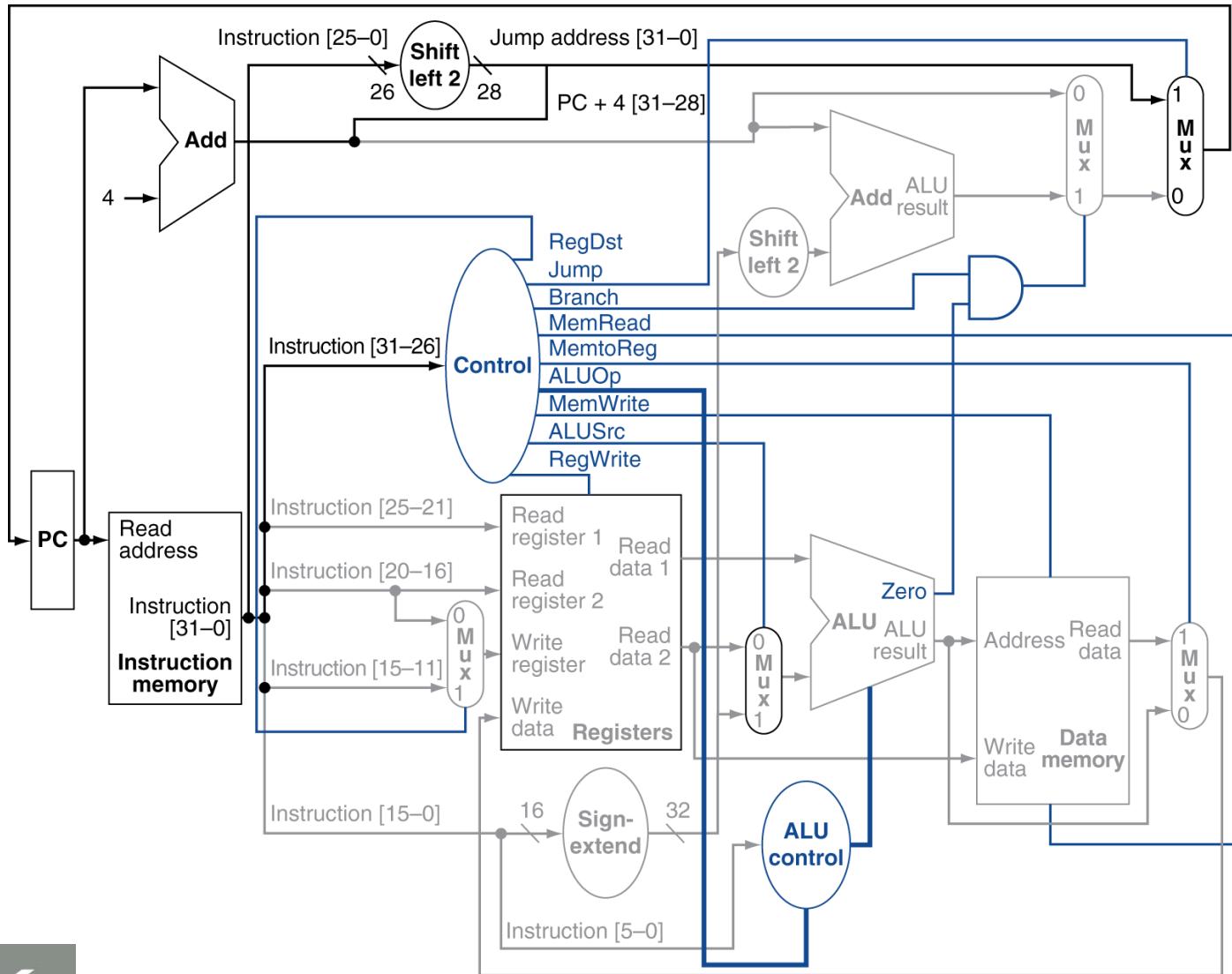

Performance

- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware

Performance Issues

- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
 - Making the common case fast
- We will improve performance by pipelining

Problems to Solve

- 4.1, 4.2, 4.4, 4.7, 4.9