

MIPS DATAPATH

FCIS Ainsams University
Spring2021

AGENDA

- Register file
- Datapath Module (R-type & I-Type instructions)
- Hands-on: Datapath Implementation

REGISTER FILE

- A register file (RF) is an array of processor registers in a central processing unit (CPU).
- In MIPS it contains 32 registers.

ra1: read register address1

ra2: read register address2


wa: write address

wd: write data



rd1: read data1

rd2: read data2

we: write enable

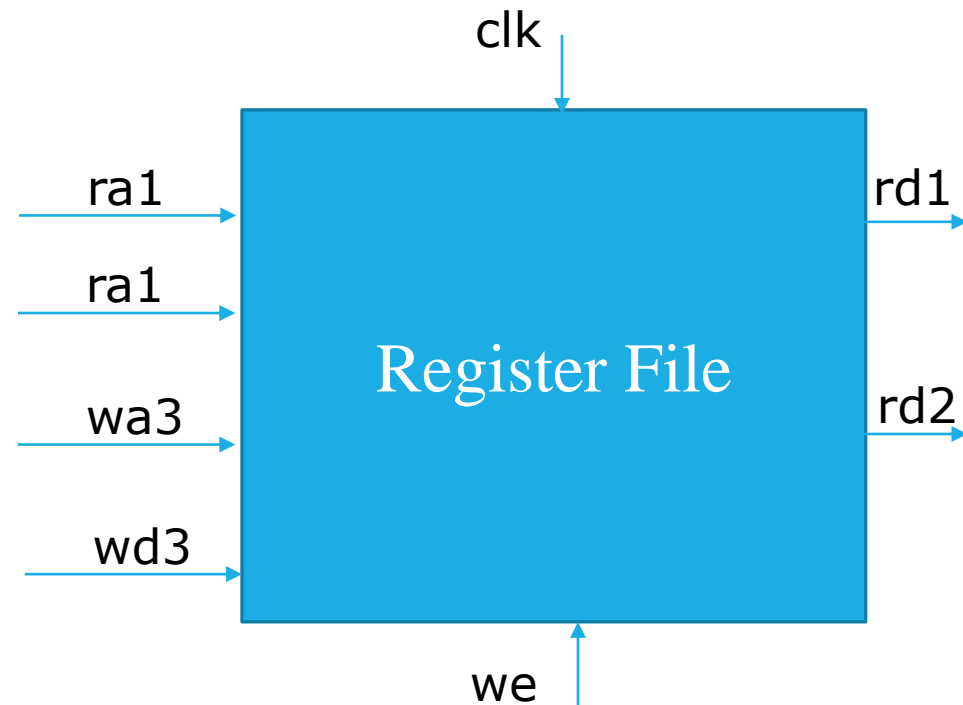


REGISTER FILE

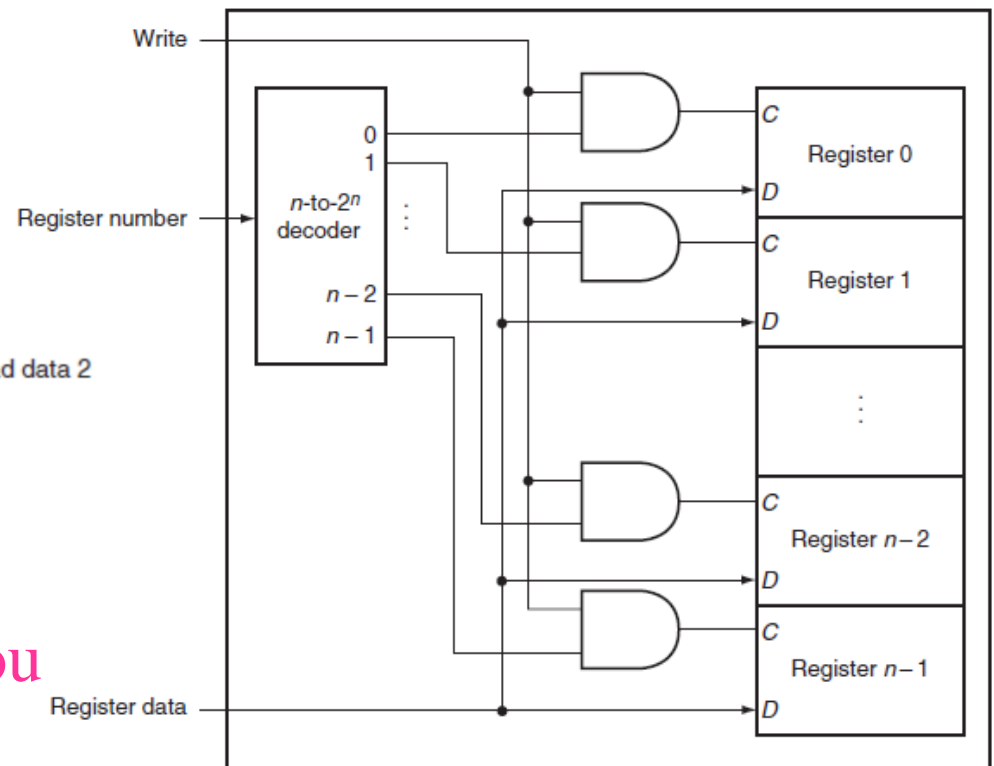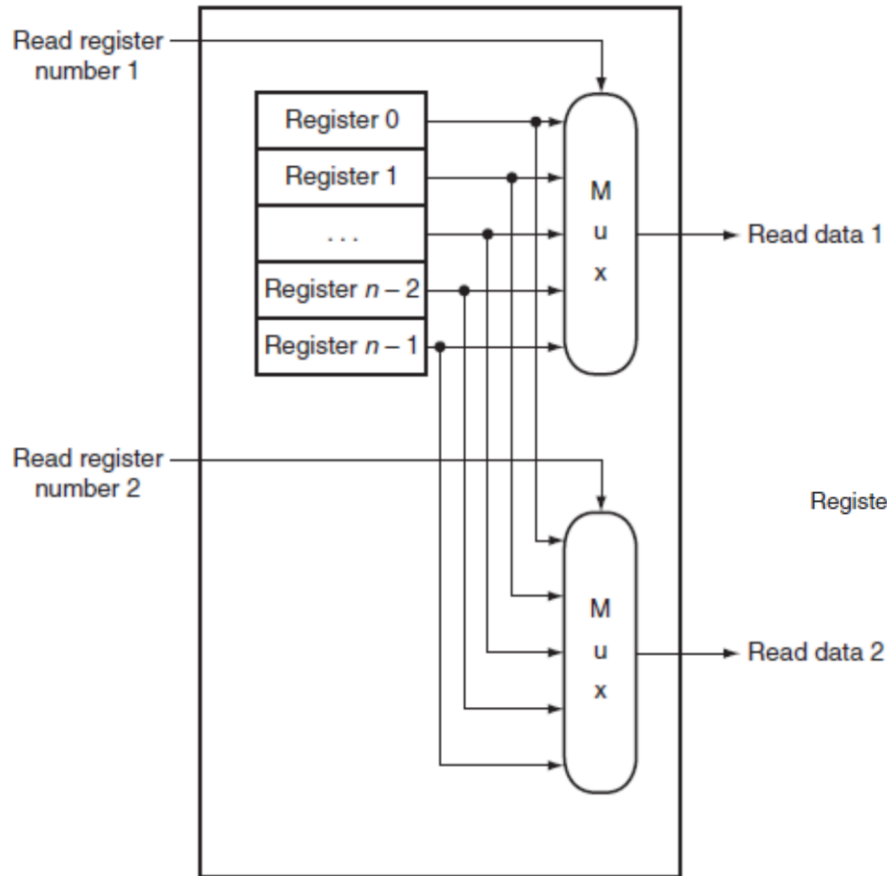

Implemented on behalf of you

DATA PATH

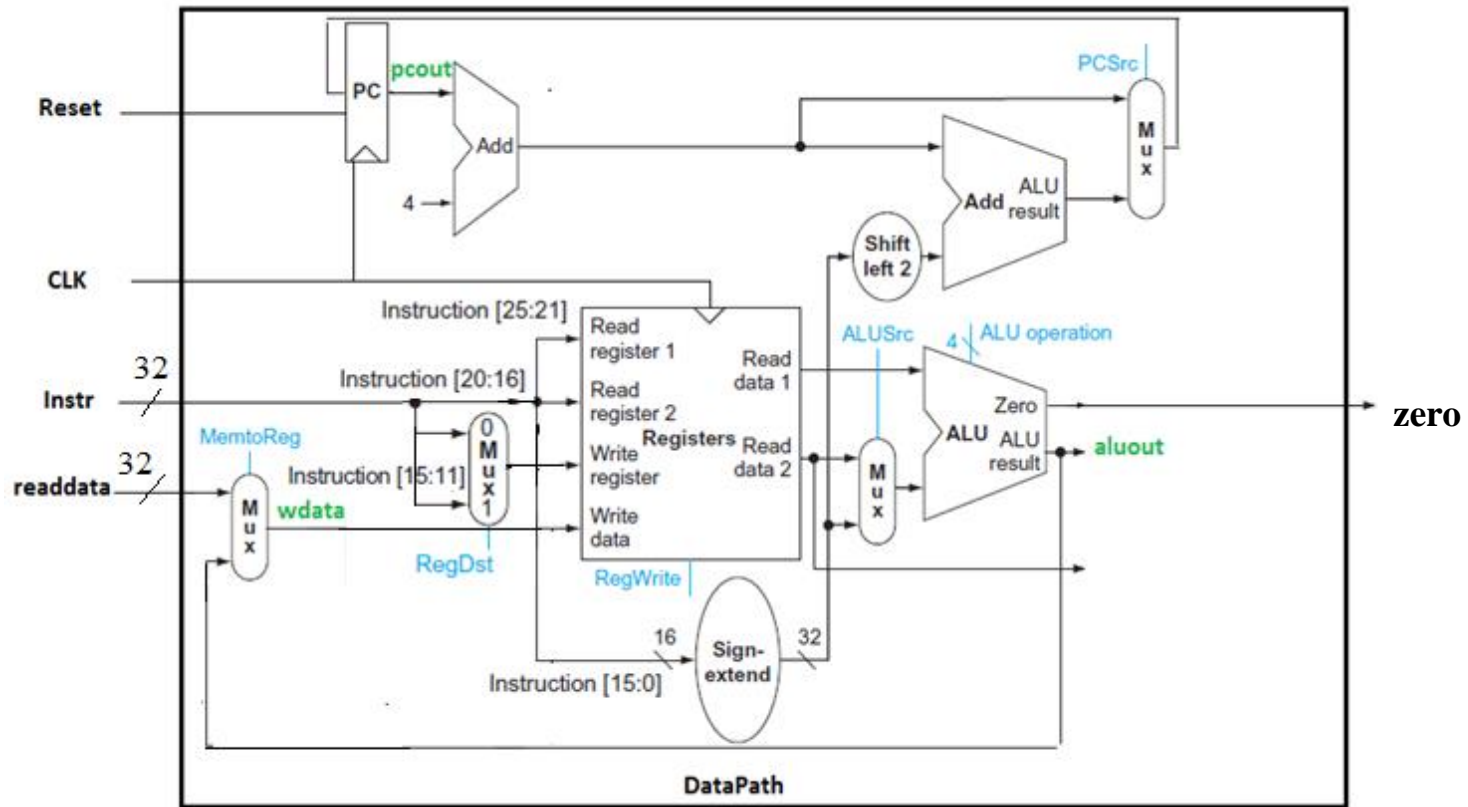

Field bit positions

31-26

25-21

20-16

15-11

10-6

5-0

No. of bits

6

5

5

5

5

6

R-type

op

rs

rt

rd

shamt

funct

I-type


op

rs

rt

16- bit immediate/address

DATA PATH

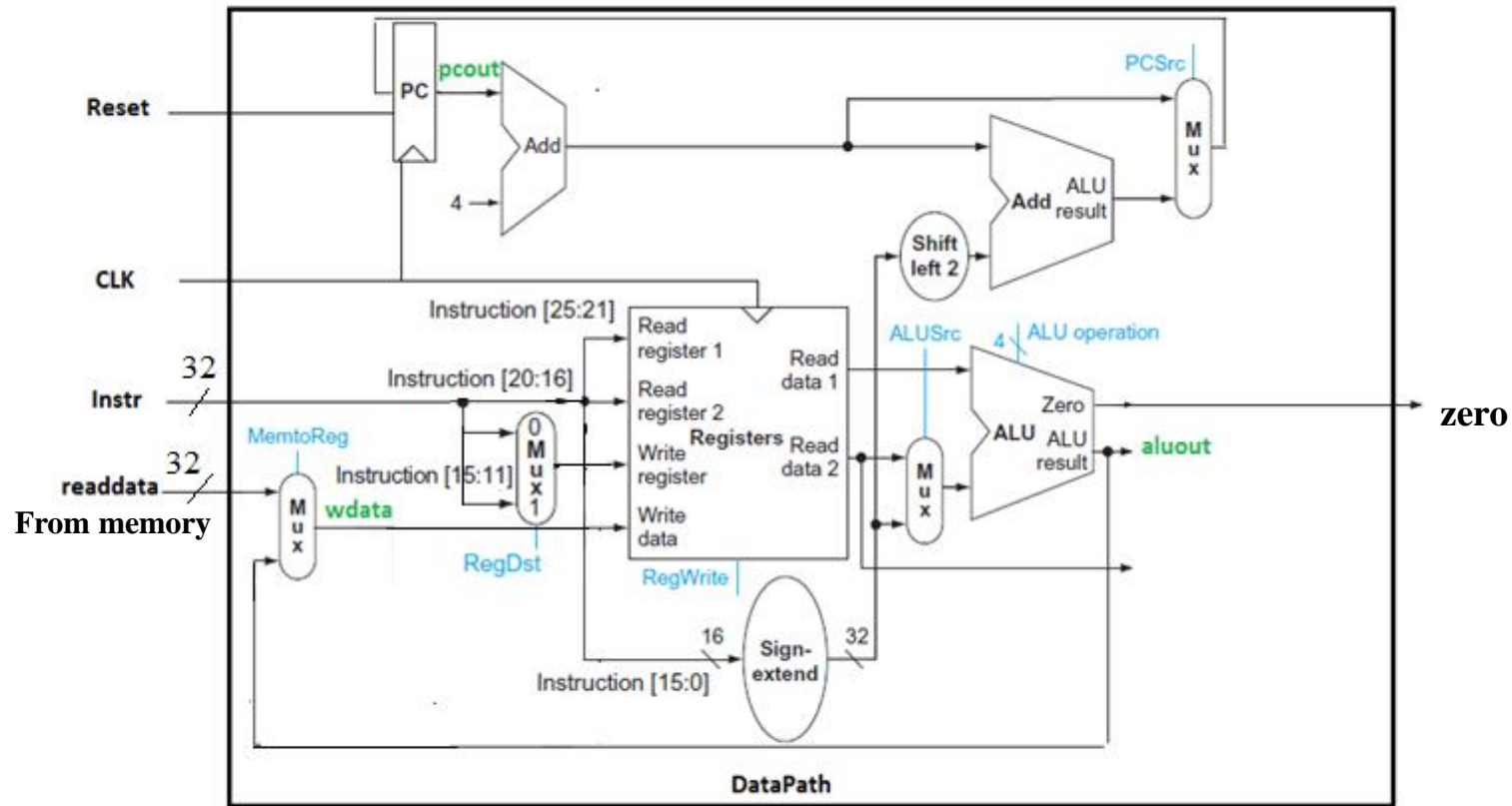

All blue controls are input

DATAPATH IMPLEMENTATION

1. Create a main module for the datapath (DataPath Entity)

```
entity datapath is -- MIPS datapath
```

```
    port(clk, reset: in STD_LOGIC;
```

```
    readdata: in STD_LOGIC_VECTOR(31 downto 0);
```

```
    instr: in STD_LOGIC_VECTOR(31 downto 0);
```

```
    memtoreg, pcsrc, alusrc, regwrite, regdst: in STD_LOGIC;
```

```
    aluoperation: in STD_LOGIC_VECTOR(2 downto 0);
```

```
    zero: out STD_LOGIC;
```

```
    pc: buffer STD_LOGIC_VECTOR(31 downto 0);
```

```
    aluout, writedata: buffer STD_LOGIC_VECTOR(31 downto 0));
```

```
end;
```

DATAPATH IMPLEMENTATION


2. add the needed vhdl files:

- Adder
- S12
- Signext
- flopr
- mux2
- Alu
- regfile

DATAPATH IMPLEMENTATION

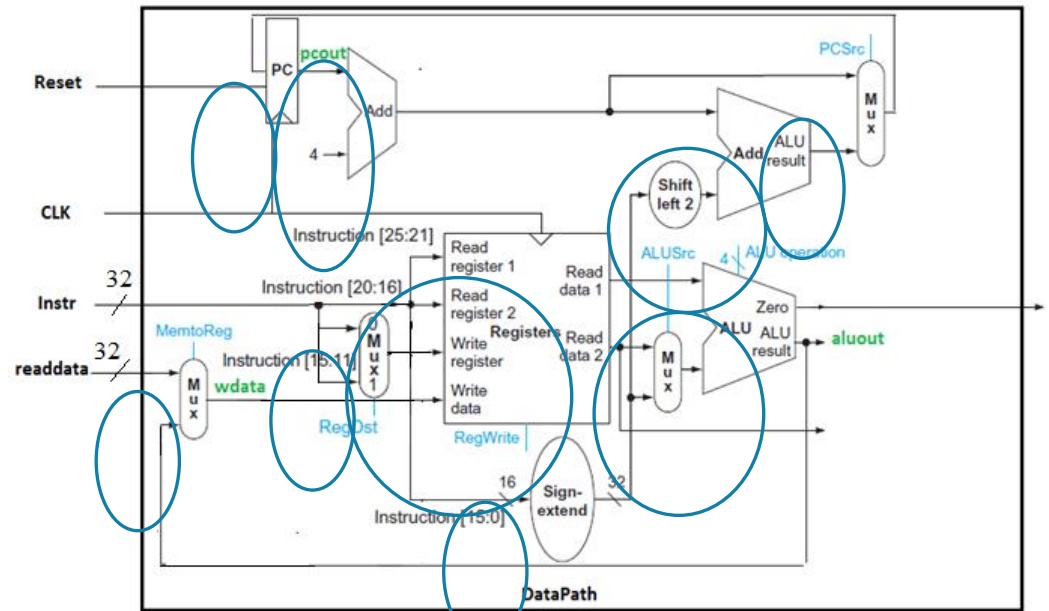2. Add the needed vhdl files you've previously implemented:

- Adder
- S12
- Signext
- flopr
- mux2
- Alu
- Regfile (given to you- attached with this ppt)



DATAPATH IMPLEMENTATION


3. Add the MIPS package created last lab: “MyPackage”. to be used while building the MIPS processor
 - Don’t forget to create a component for the RegisterFile

```
component regfile
    port(clk: in STD_LOGIC;
         we: in STD_LOGIC;
         ra1, ra2, wa: in STD_LOGIC_VECTOR(4 downto 0);
         wd: in STD_LOGIC_VECTOR(31 downto 0);
         rd1, rd2: out STD_LOGIC_VECTOR(31 downto 0));
end component;
```

DATAPATH IMPLEMENTATION

4. Behavior of the module

I. Will we need some signals

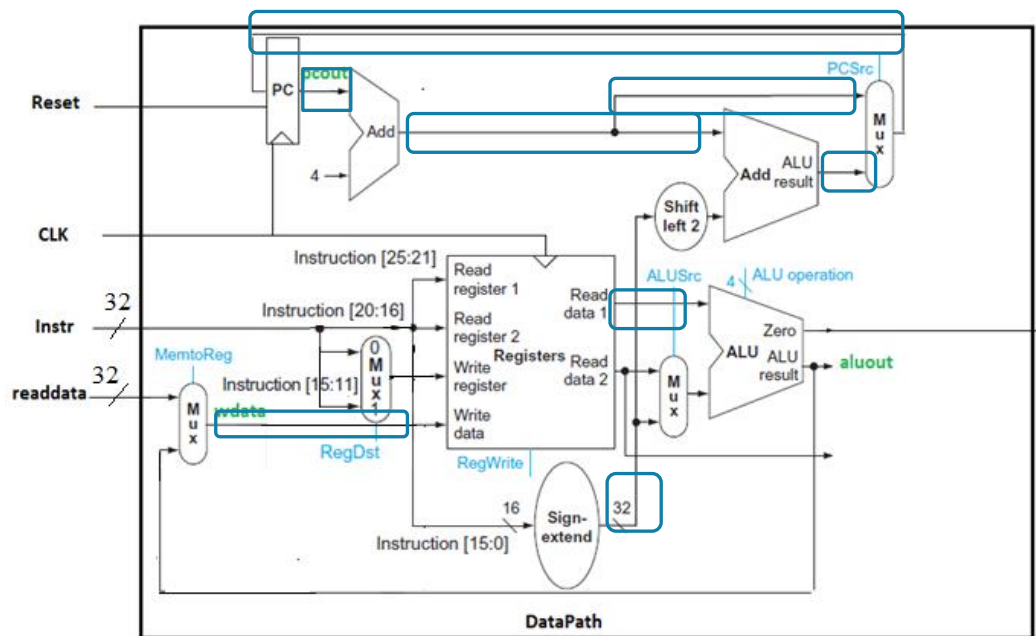

DATAPATH IMPLEMENTATION

4. Behavior of the module


I. Will we need some signals

```
signal pcnext, pcplus4,pcbranch: STD_LOGIC_VECTOR(31 downto 0);
signal signimm, signimmsh: STD_LOGIC_VECTOR(31 downto 0);
signal srca, srcb, result: STD_LOGIC_VECTOR(31 downto 0);
signal wdata: STD_LOGIC_VECTOR(31 downto 0);
signal writereg: STD_LOGIC_VECTOR(4 downto 0);
```

DATAPATH IMPLEMENTATION

4. Behavior of the module

II. next PC logic

 


```
begin
-- next PC logic
pcreg: flopr generic map(32) port map(clk, reset, pcnext, pc);
pcadd1: adder port map(pc, X"00000004", pcplus4);
immsh: sl2 port map(signimm, signimmsh);
pcadd2: adder port map(pcplus4, signimmsh, pcbranch);
pcbrmux: mux2 generic map(32) port map(pcplus4, pcbranch, pcsrc, pcnext);
```

DATAPATH IMPLEMENTATION

4. Behavior of the module
 - III. register file logic

Your turn?

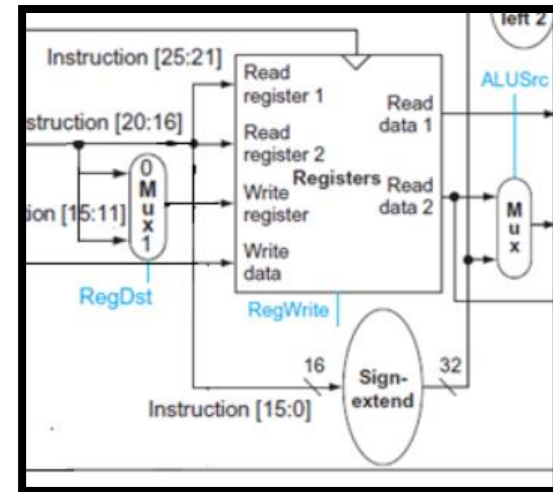


DATAPATH IMPLEMENTATION

4. Behavior of the module


IV. ALU logic

Your turn?

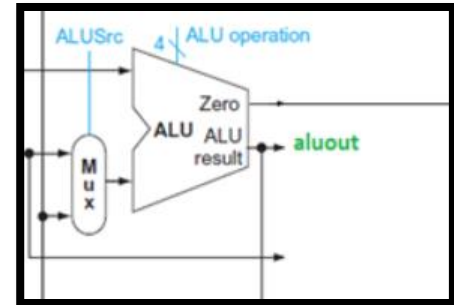

DATAPATH IMPLEMENTATION

RTL of Datapath

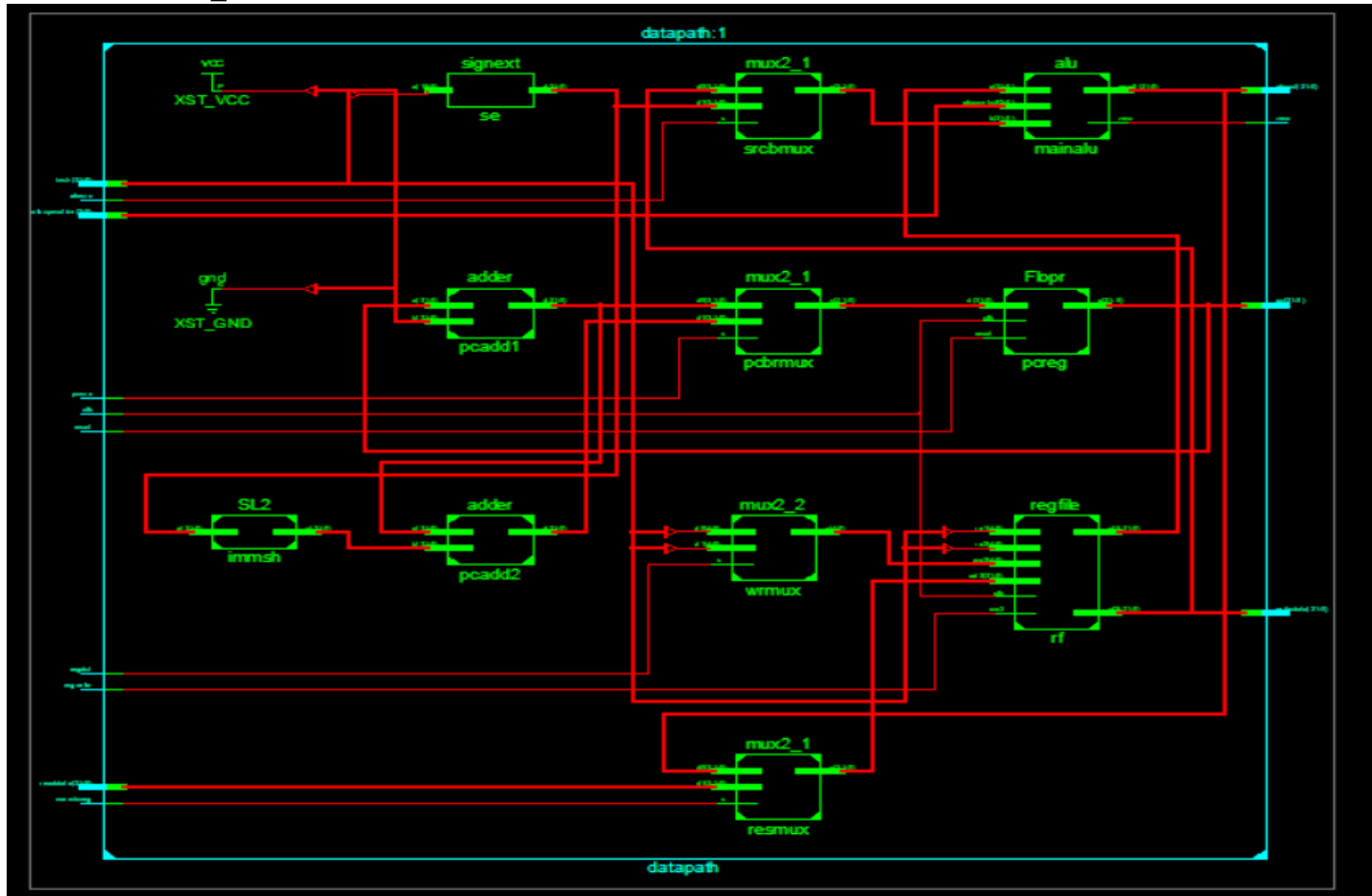



Thanks