

Chapter 4

The Processor

Dr. Randa Mohamed

Agenda

- Introduction
- Logic design basics
- MIPS Datapath: R-Type & I-Type

Introduction

- Processor design is composed of 2 modules:
Datapath and Control
- We will examine
 1. Two MIPS implementations
 - A simplified version (Single cycle MIPS)
 - A more realistic pipelined version (Pipelined MIPS)
 2. Implementation that supports
 - R-type instructions, like ADD, SUB
 - I-type instructions LW, SW
 - Conditional branch instruction BEQ
 - J-type branch instruction J


Logic Design Basics

- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational element
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information

Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 



- Arithmetic/Logic Unit

- $Y = F(A, B)$

 



Sequential Elements

  - Stores data in a circuit
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1



Sequential Elements

  
- Storing with write control
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later




Building a Datapath

- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design


Datapath

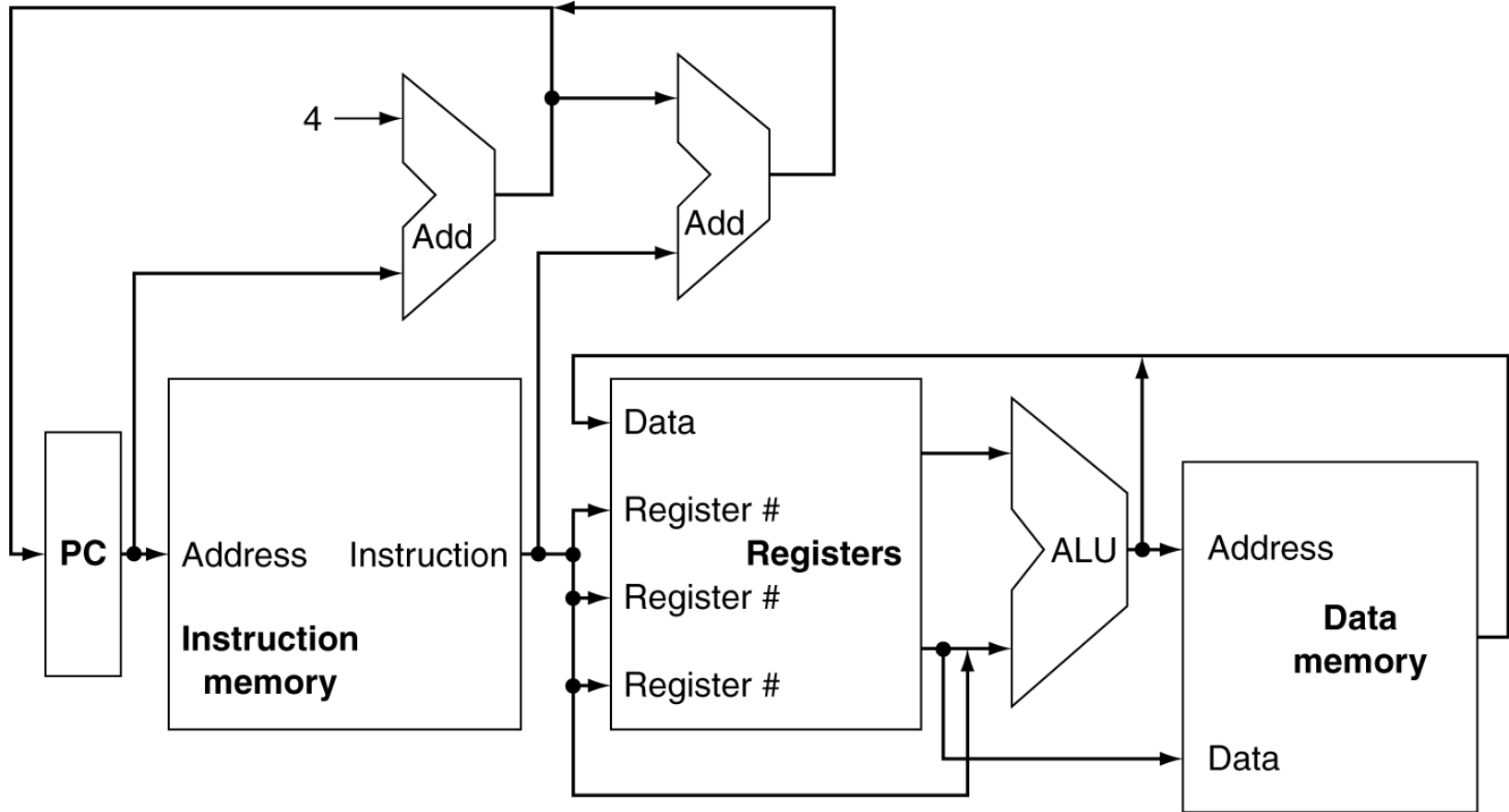


Datapath

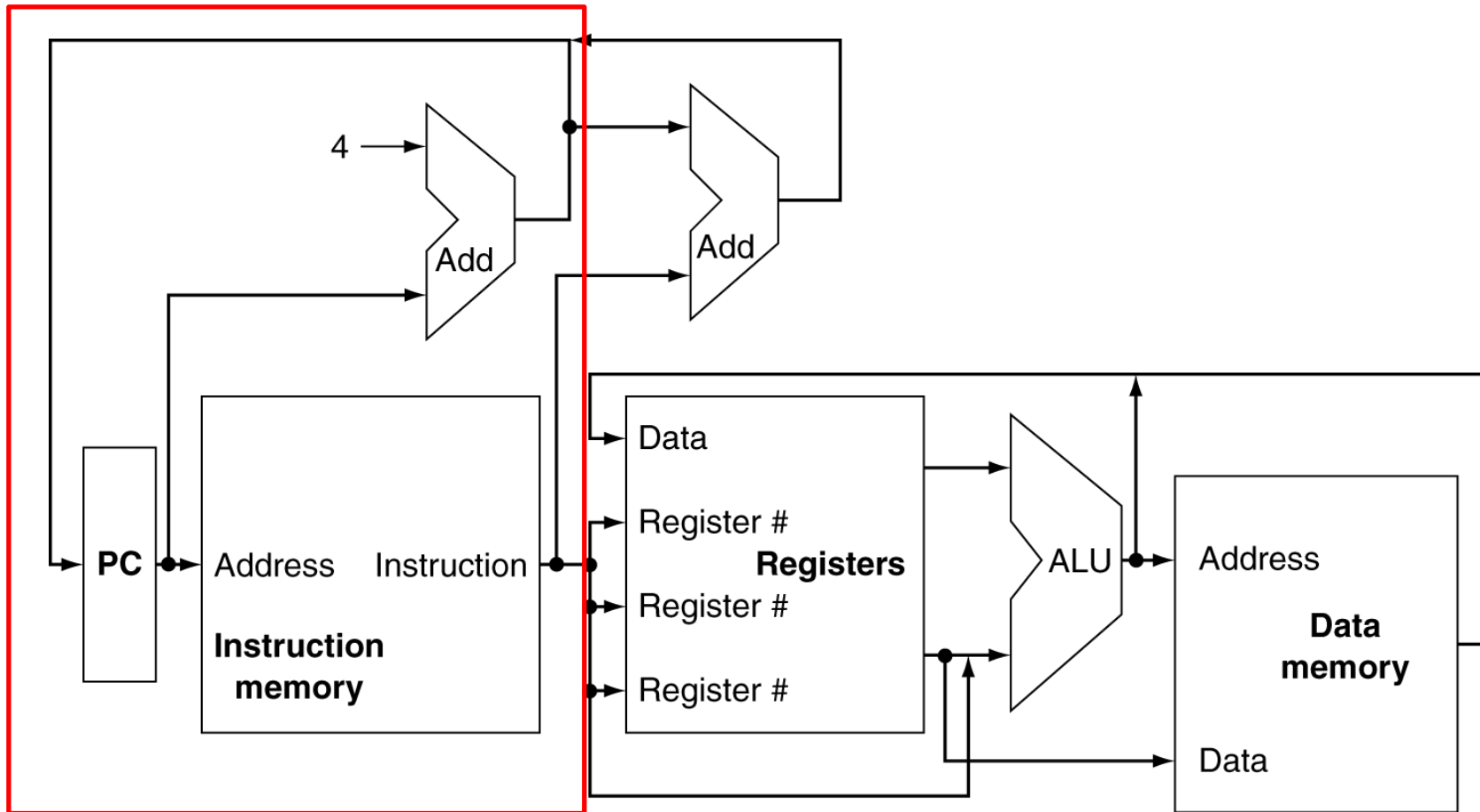

Instruction Fetch

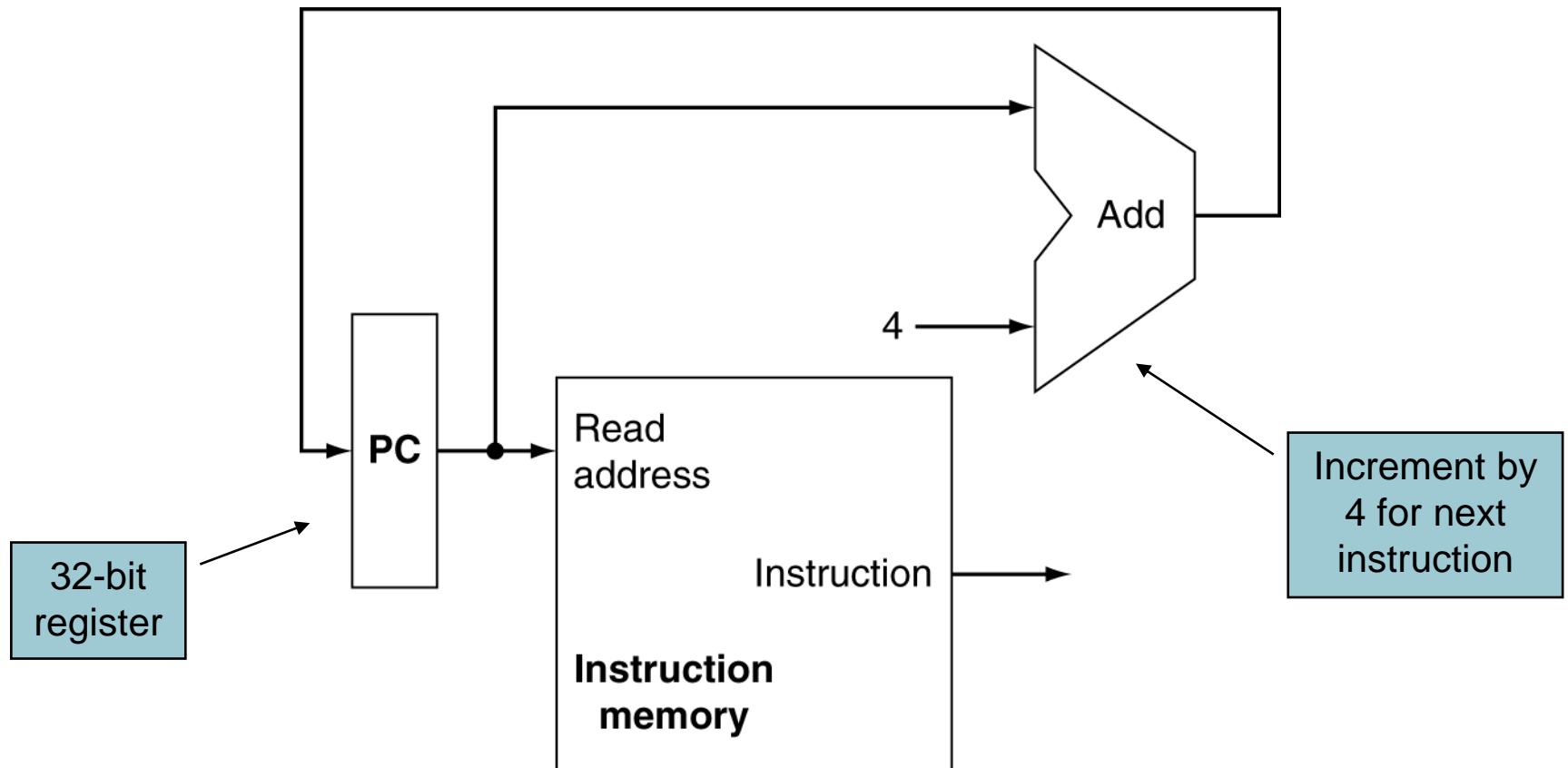


Instruction Fetch

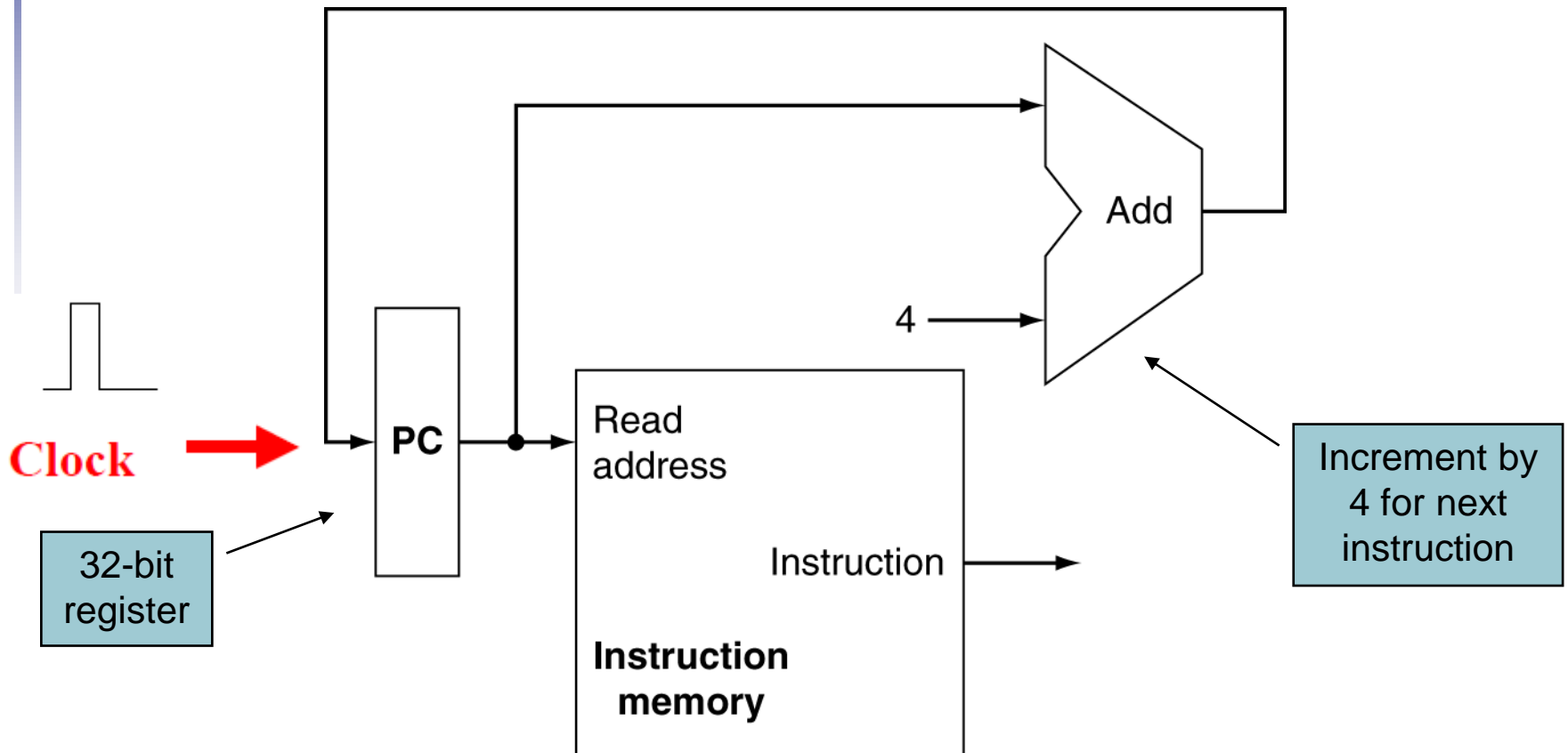

Instruction Fetch



Field bit positions	31-26	25-21	20-16	15-11	10-6	5-0
No. of bits	6	5	5	5	5	6
R-type	op	rs	rt	rd	shamt	funct
I-type	op	rs	rt	16- bit immediate/address		

R-Format Instructions


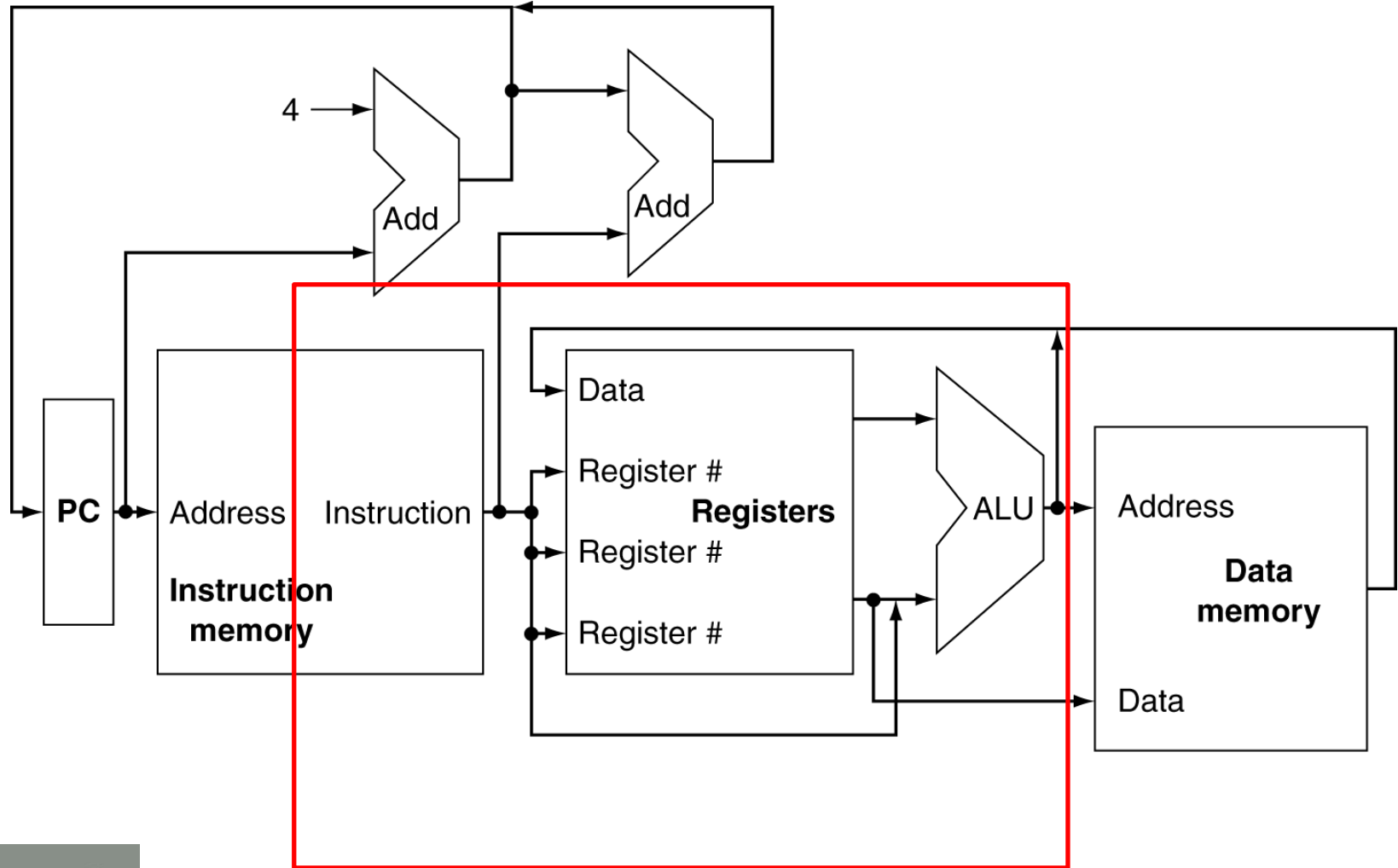


R-Format Instructions

 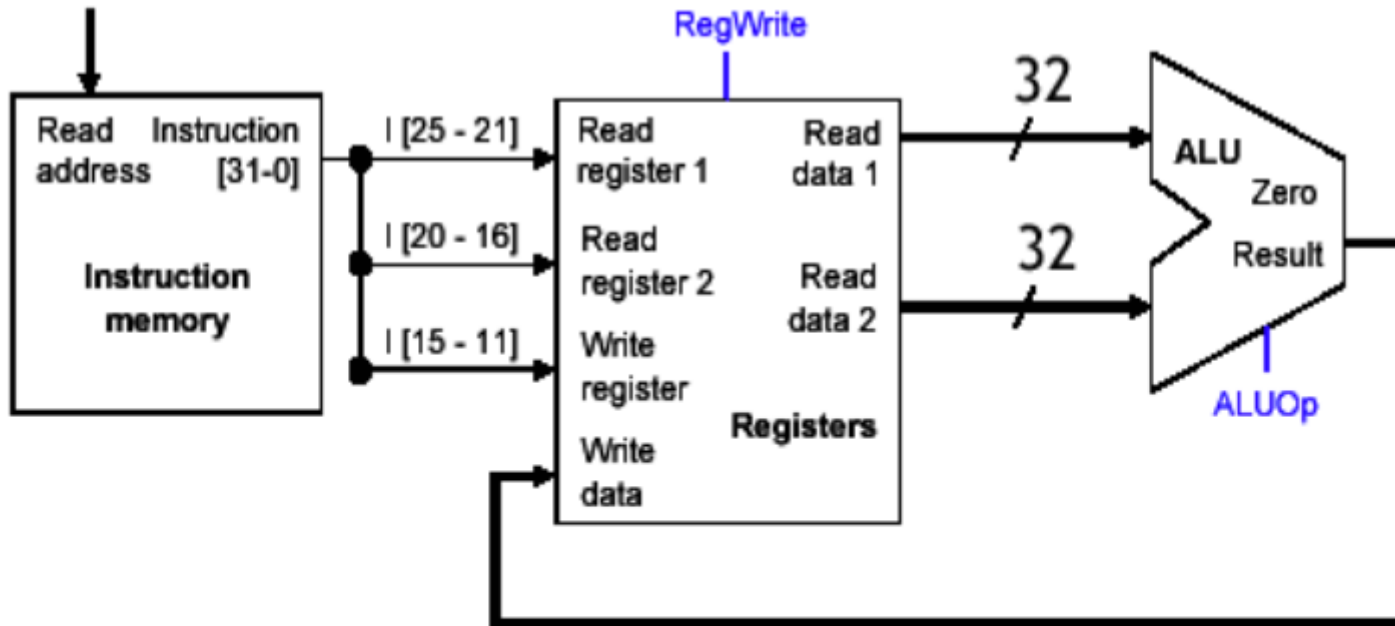
- Read two source register operands (defined by rs,rt)
- Perform arithmetic/logical operation
- Write result in destination register (defined by rd)




Register File

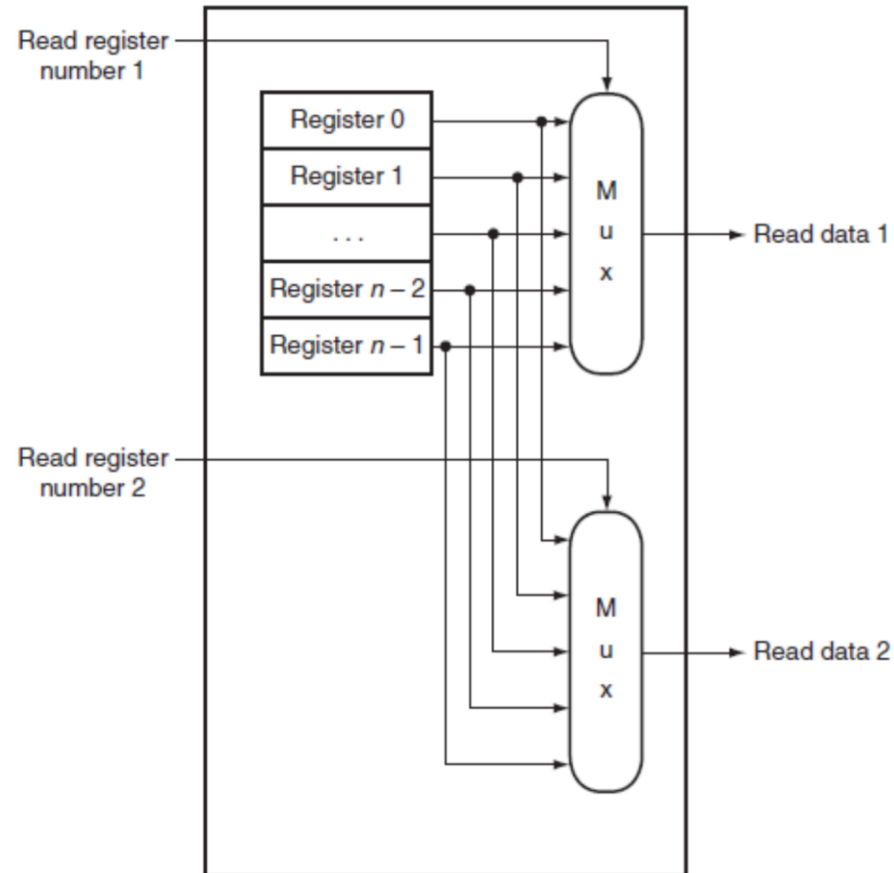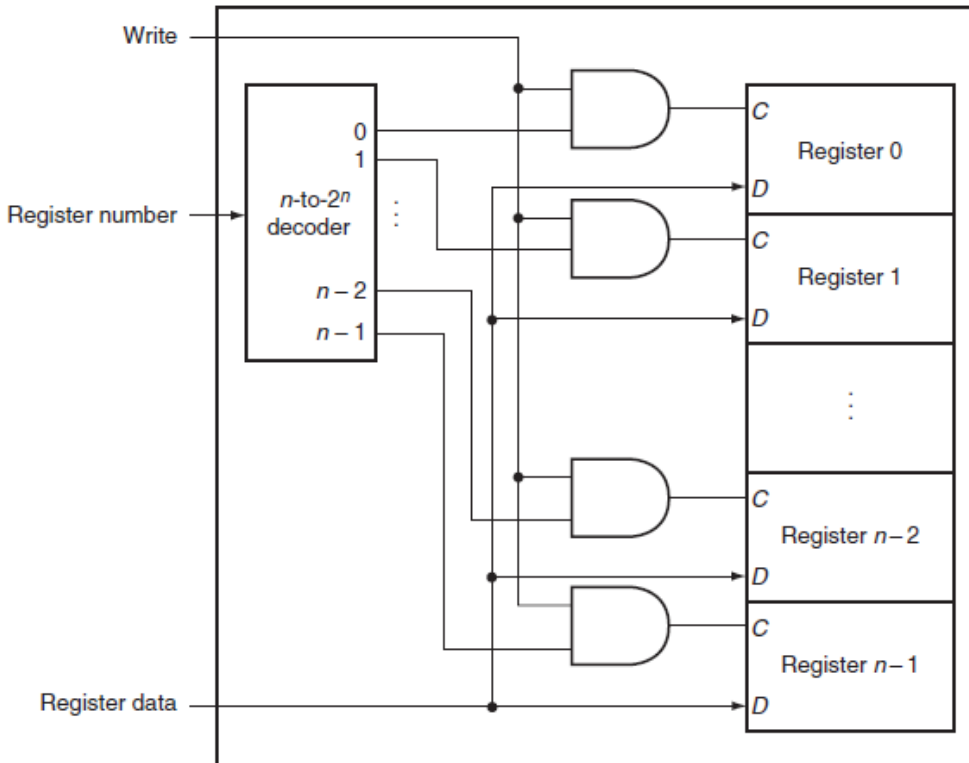

ALU

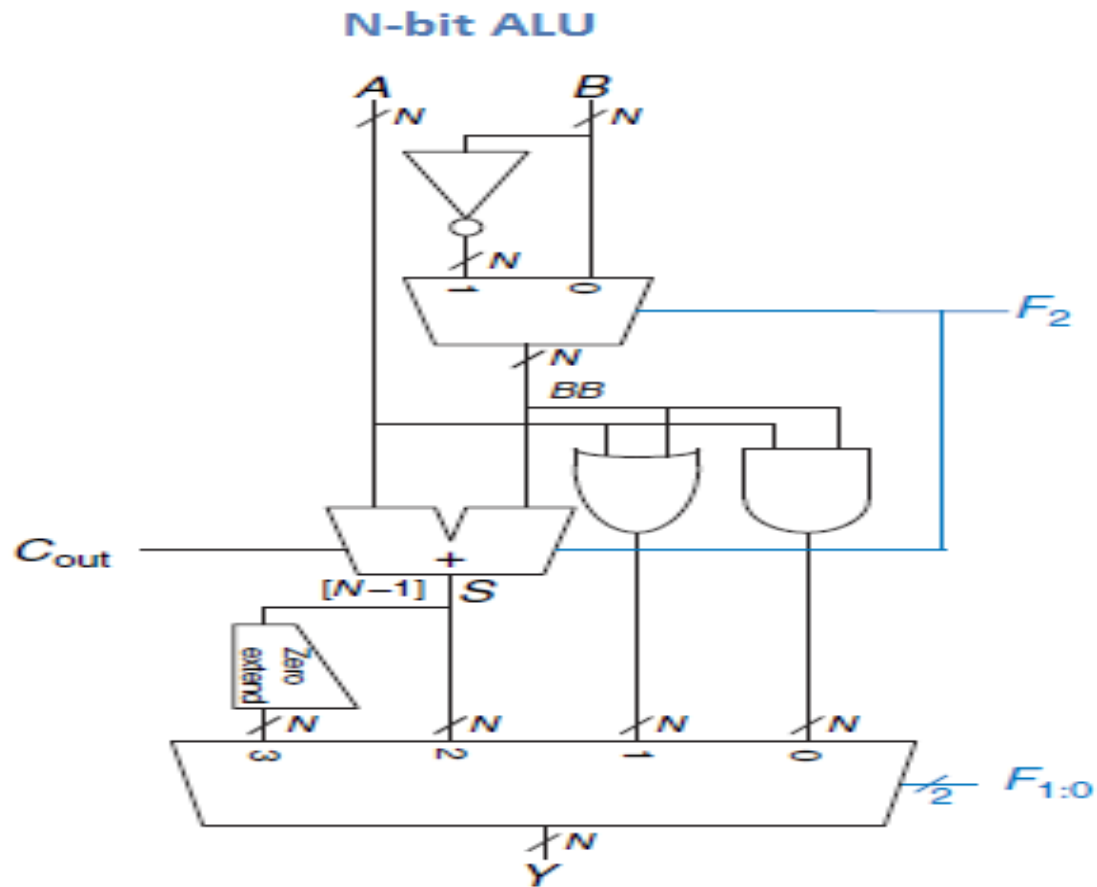


Load/Store Instructions

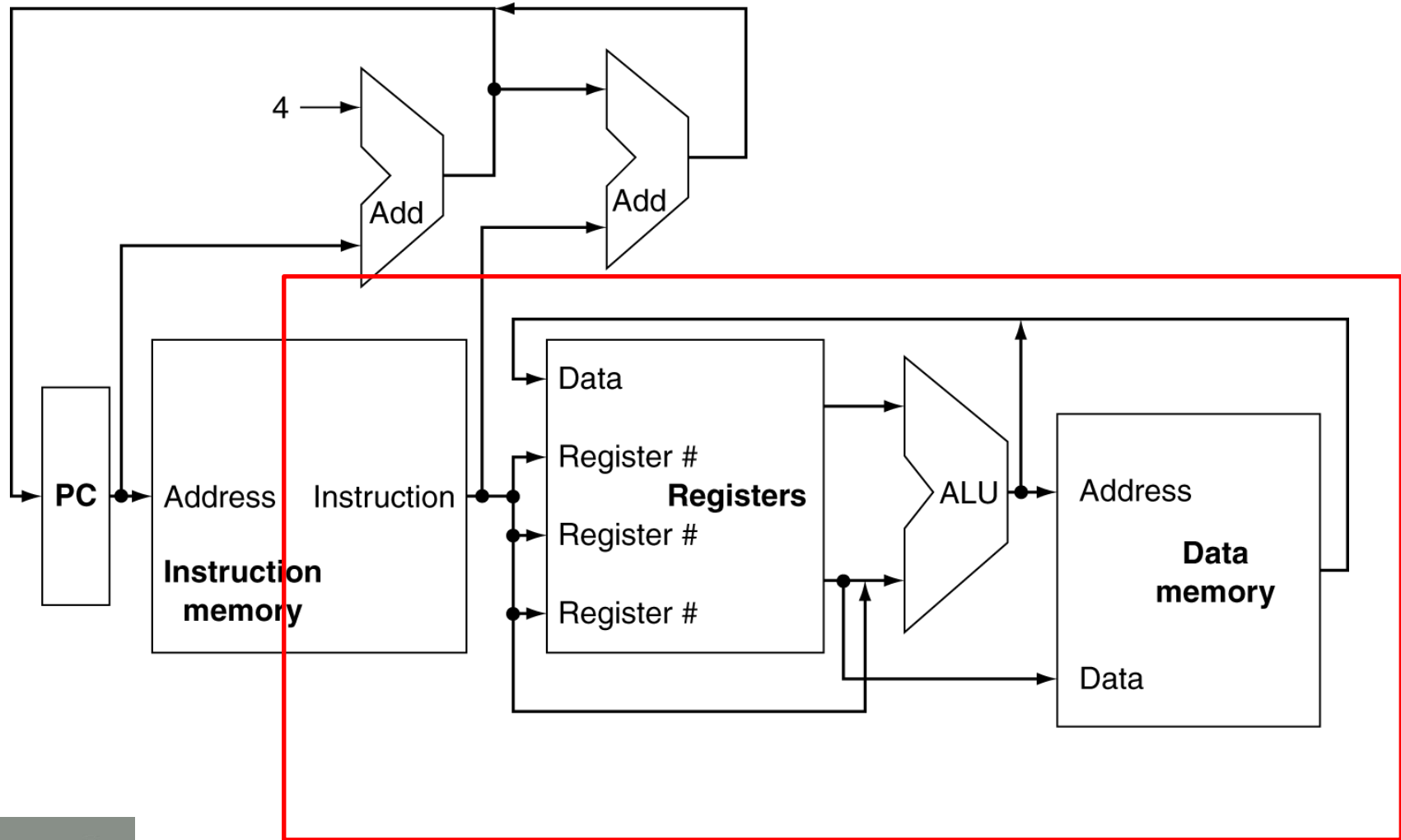


Load/Store Instructions

 - To read from the data memory, set Memory read = 1
- To write into the data memory, set Memory write = 1



a. Data memory unit


 


b. Sign extension unit

Load Instruction


- Read register operands & calculate address using 16-bit offset

What parts of R-type are altered?

 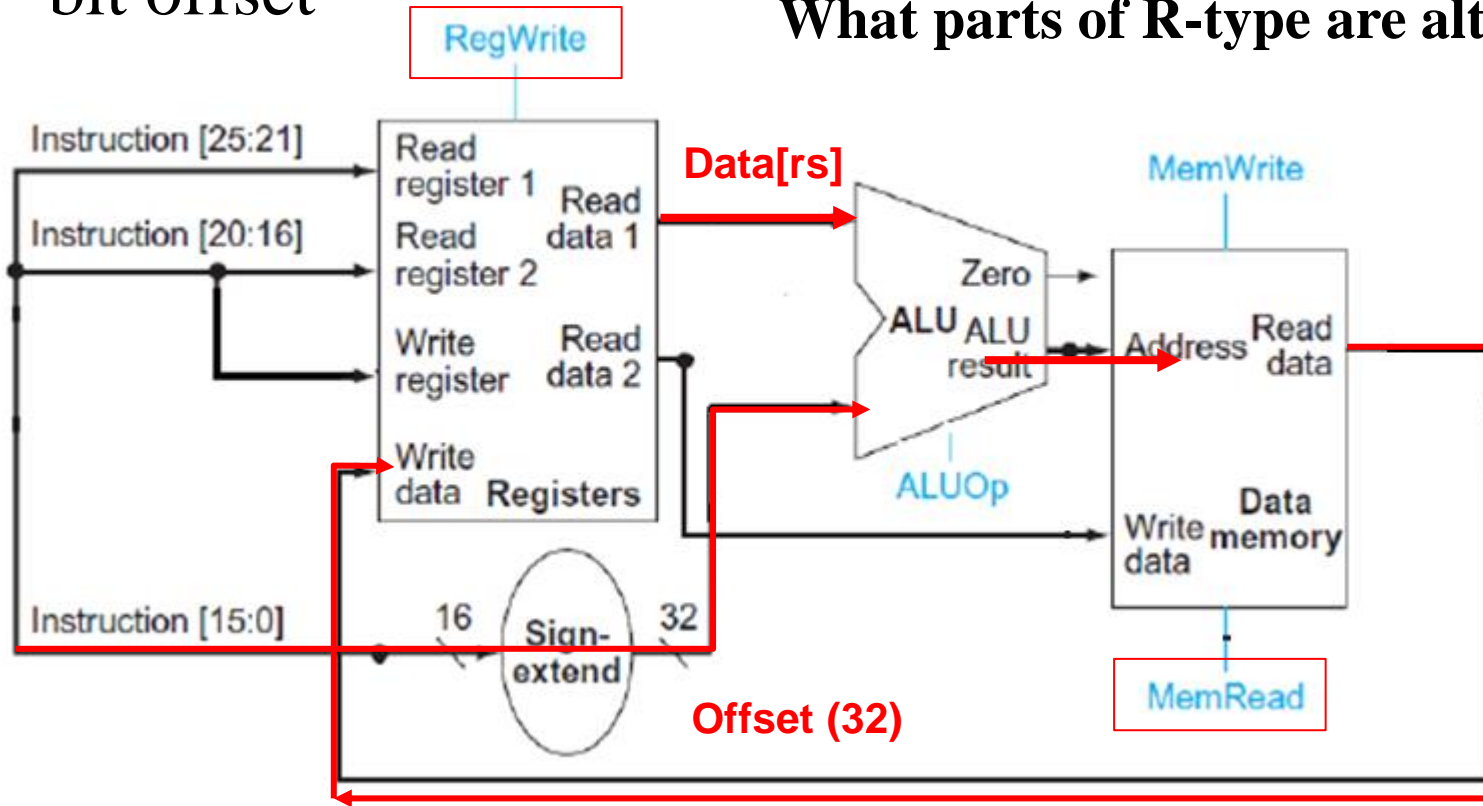


R-Type/Load Instruction

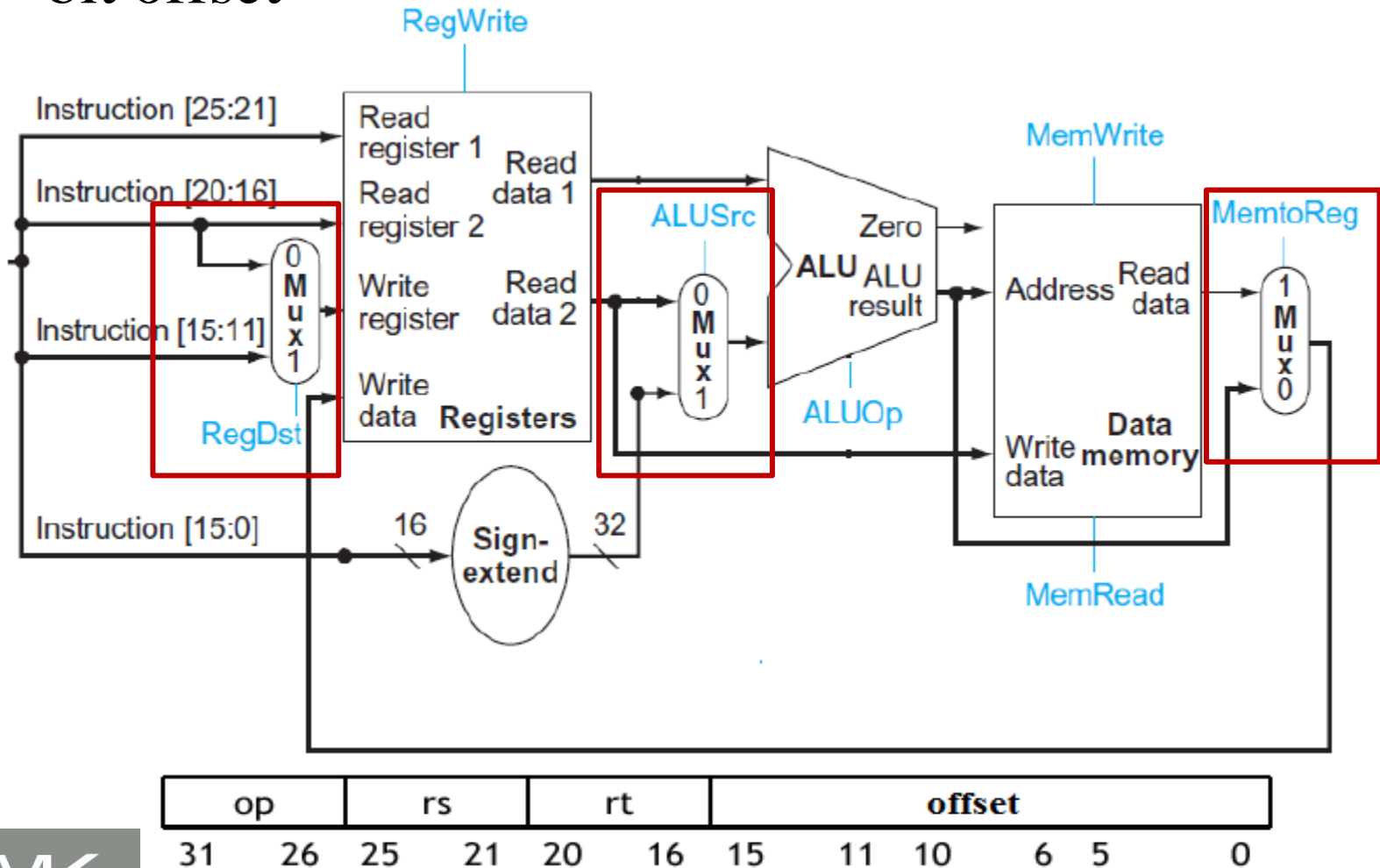- Read register operands & calculate address using 16-bit offset




Store Instruction

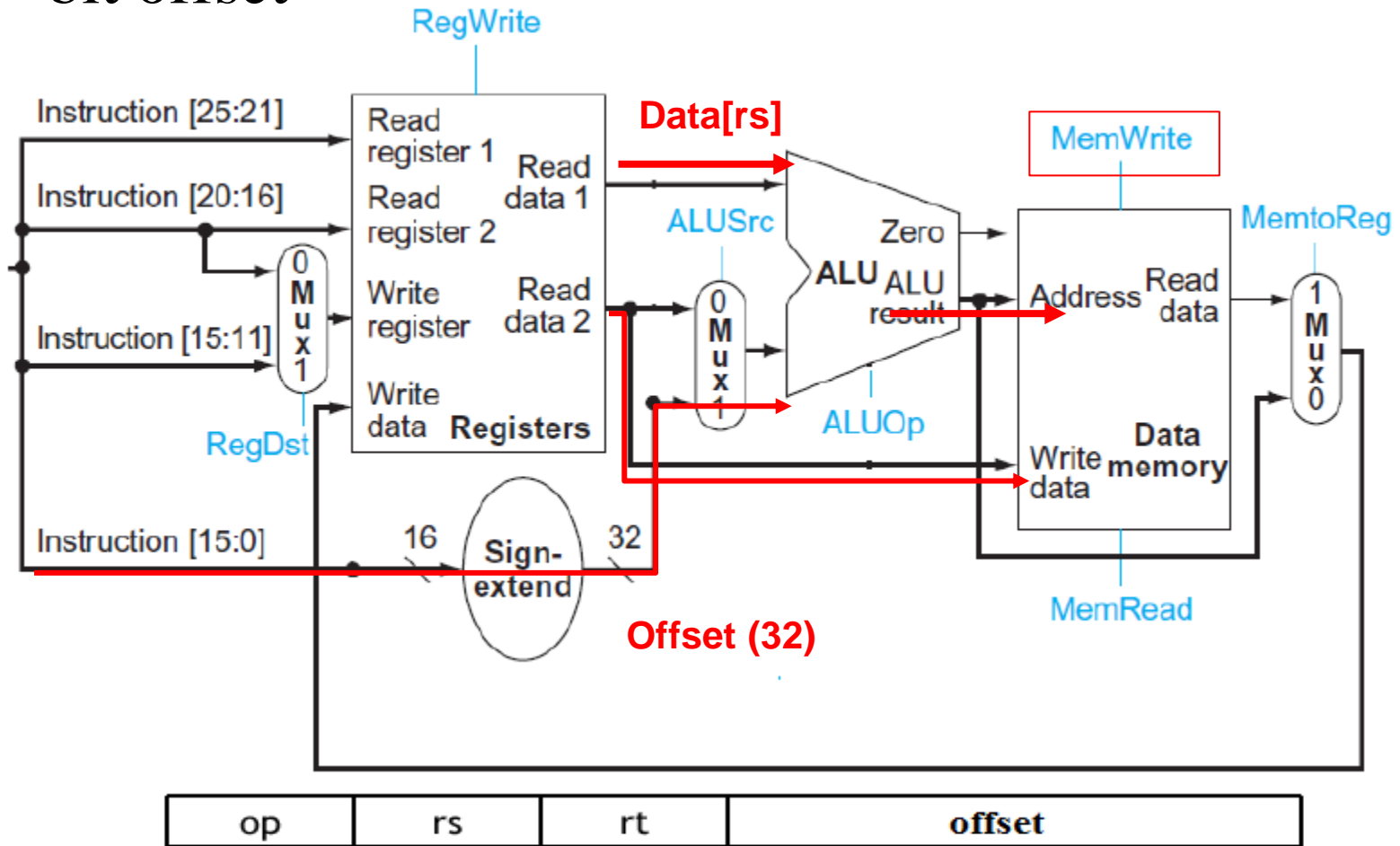- Read register operands & calculate address using 16-bit offset





R-Type/Load/Store Datapath

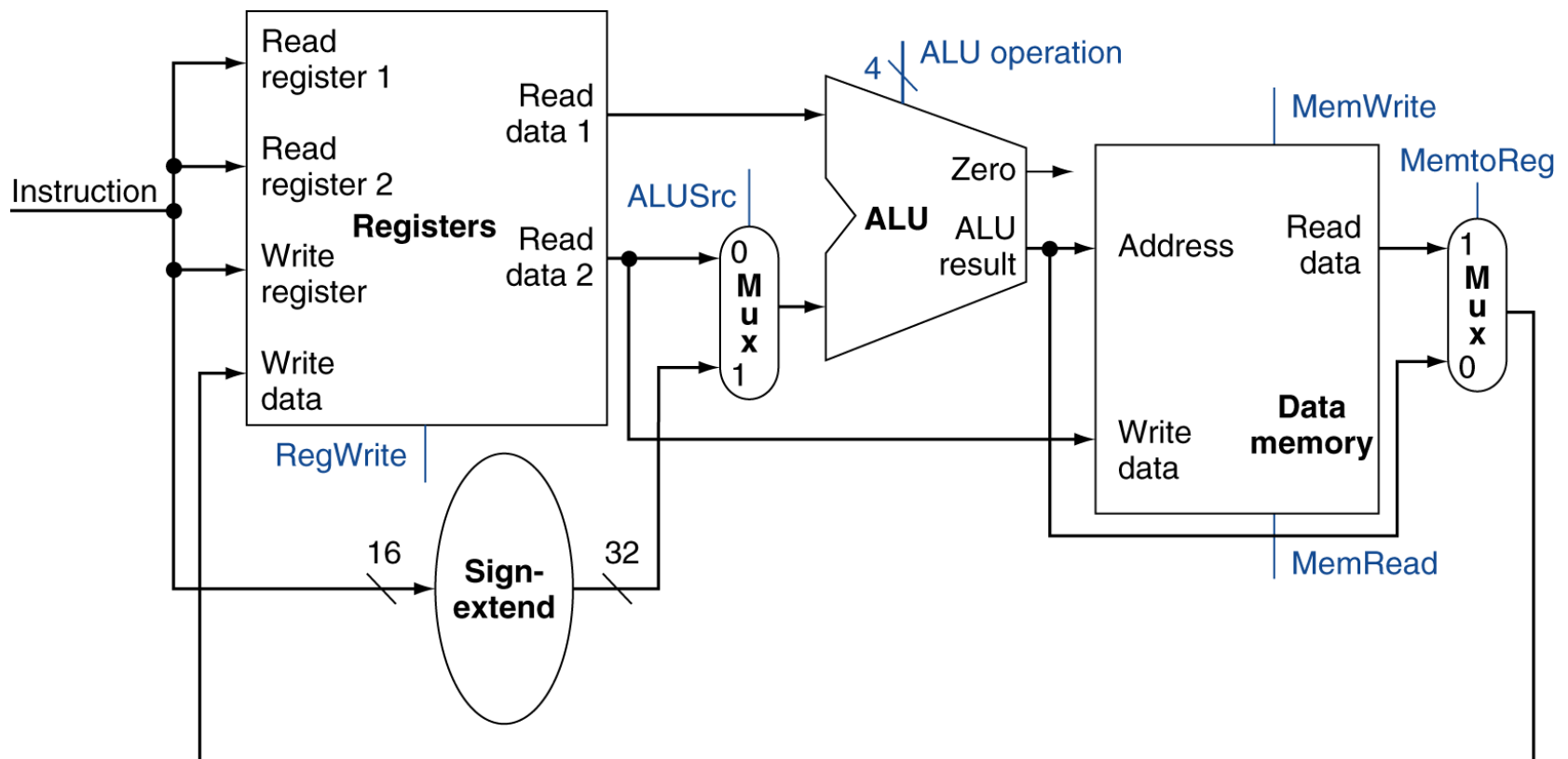


Branch Instructions

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address ($PC + 4 + Add \times 4$)
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to $PC + 4$
 - Already calculated by instruction fetch


Branch Instructions

 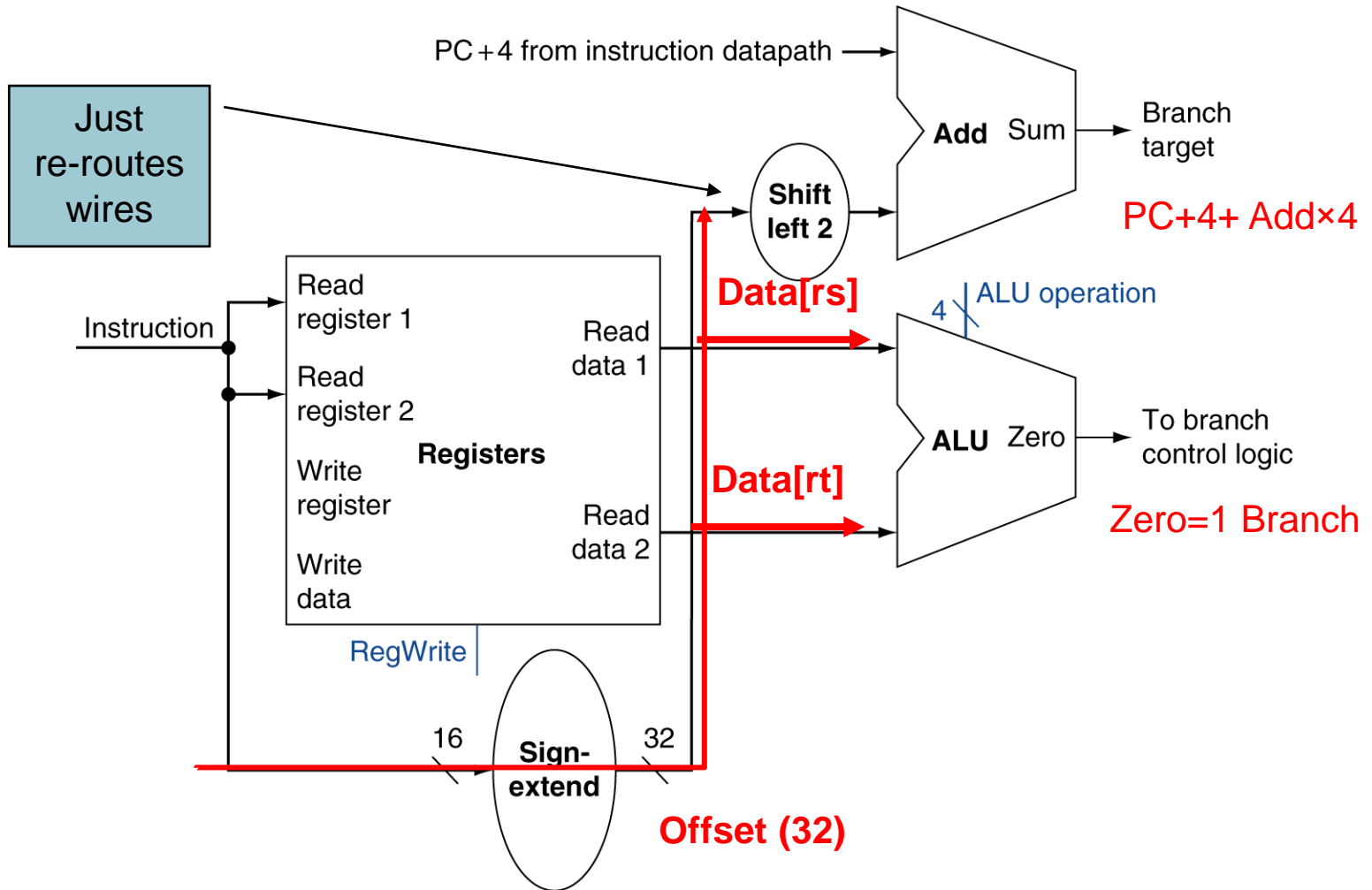


Full Datapath

 


Full Datapath: R-Type

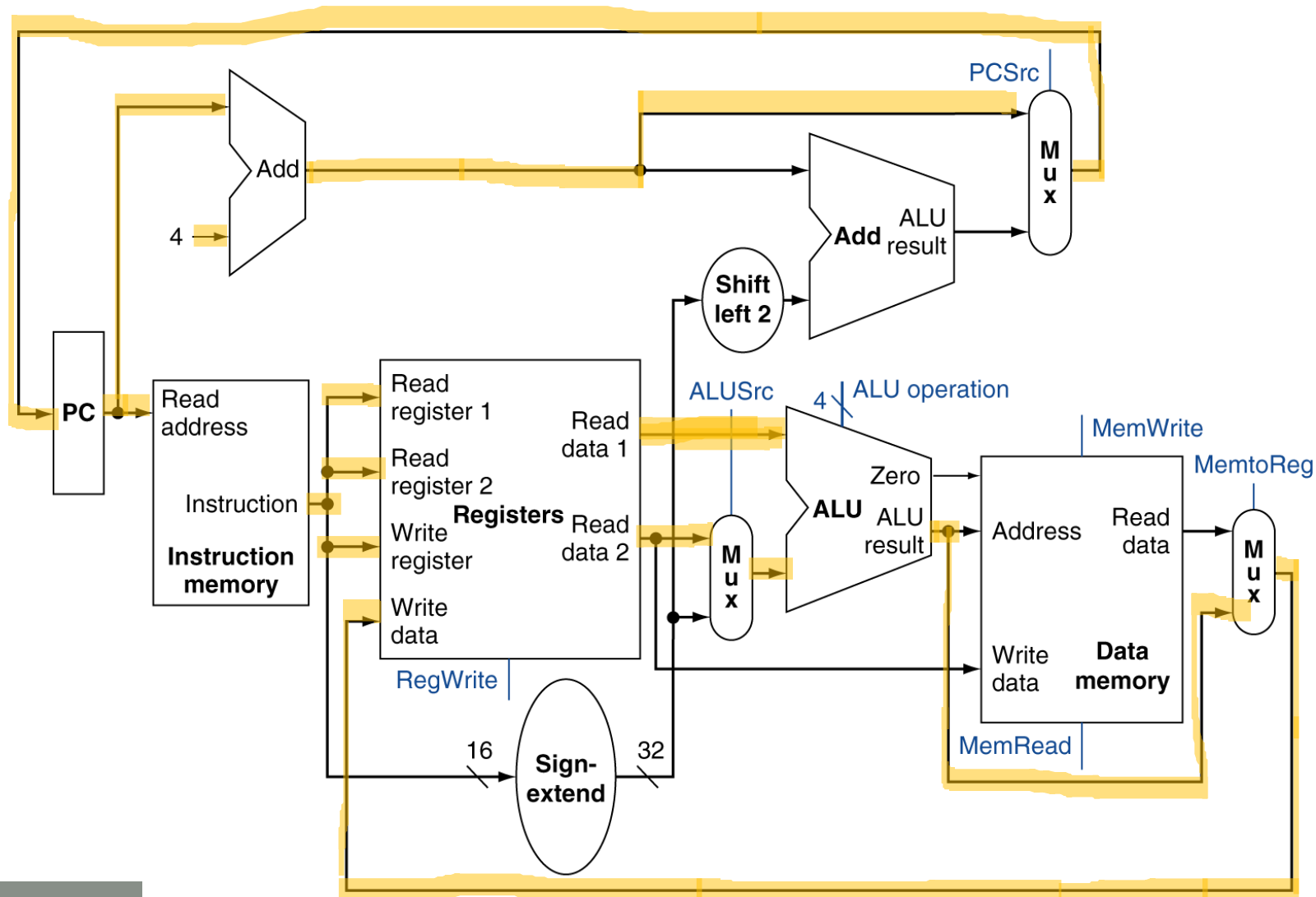


Full Datapath: I-Type (Load)

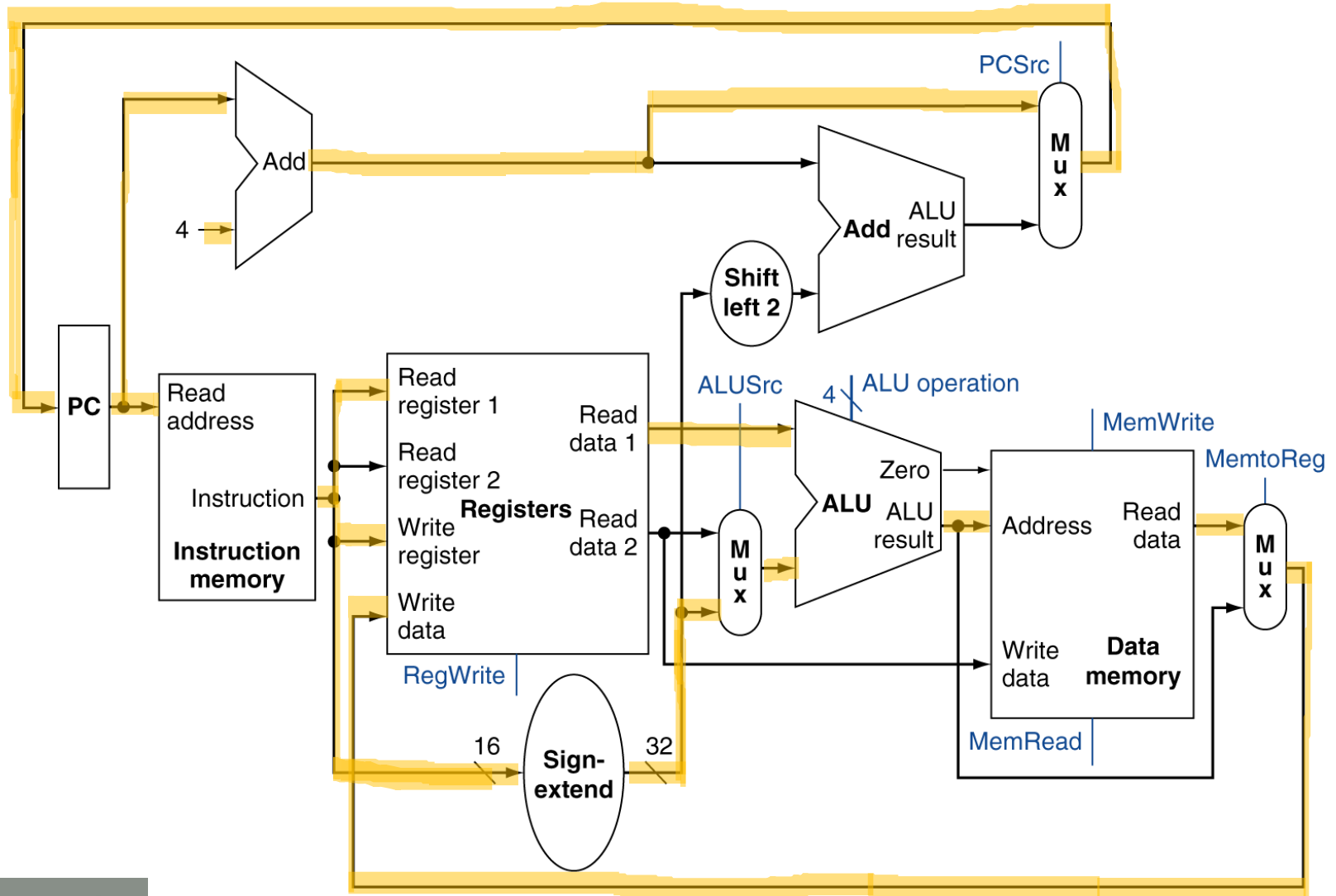


Full Datapath: I-Type (Store)

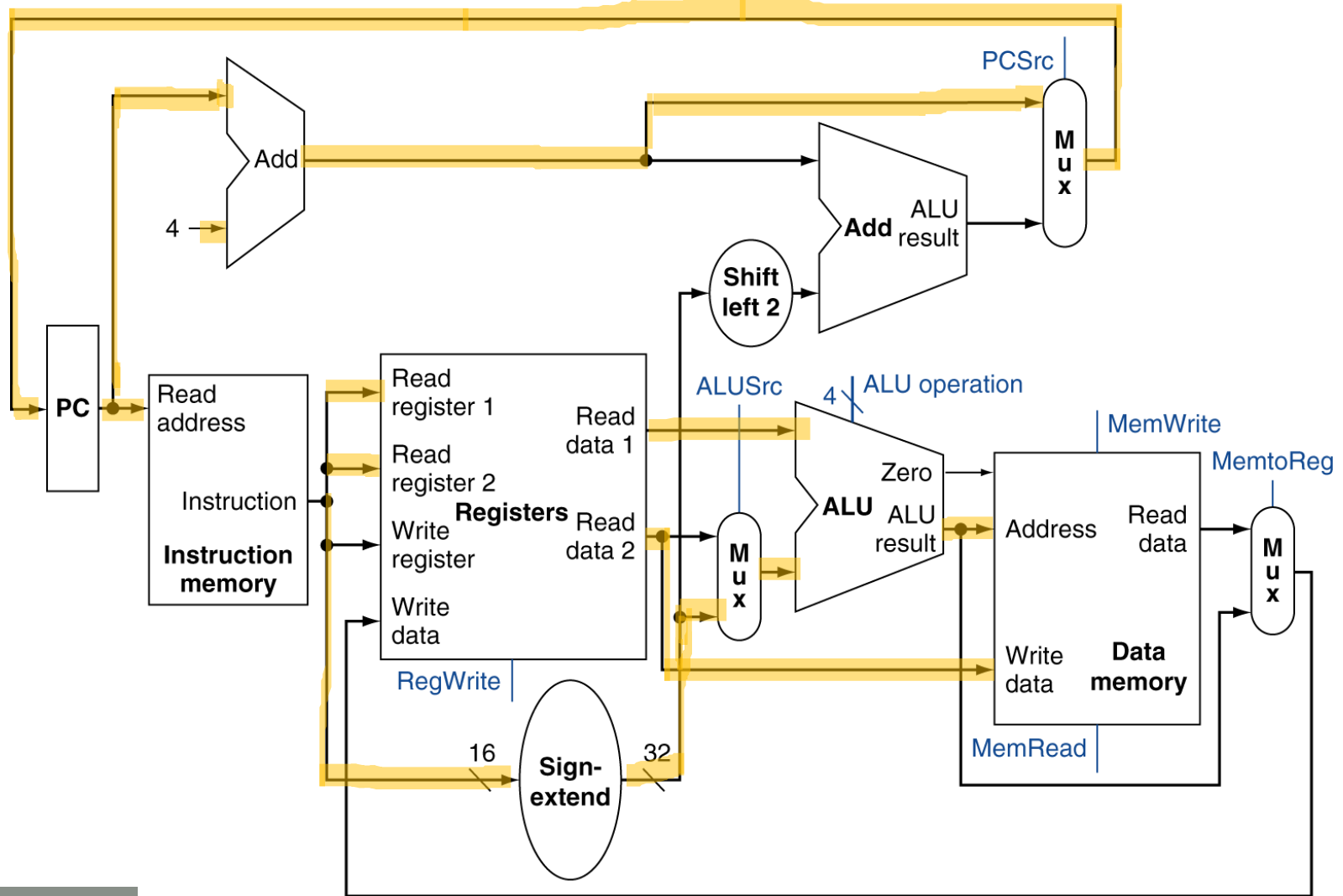

Full Datapath: I-Type (Beq:T)

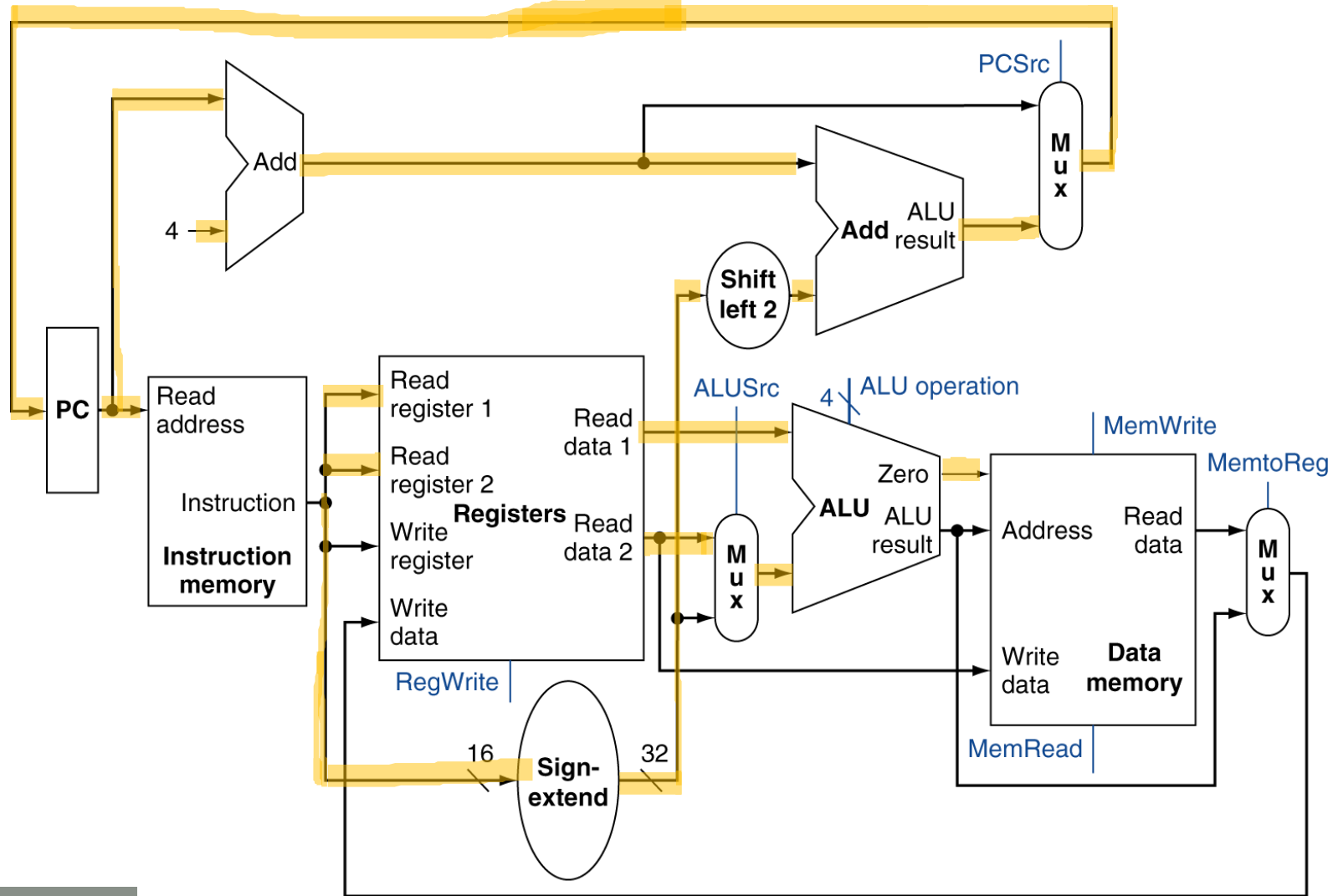

Full Datapath: I-Type (Beq:F)

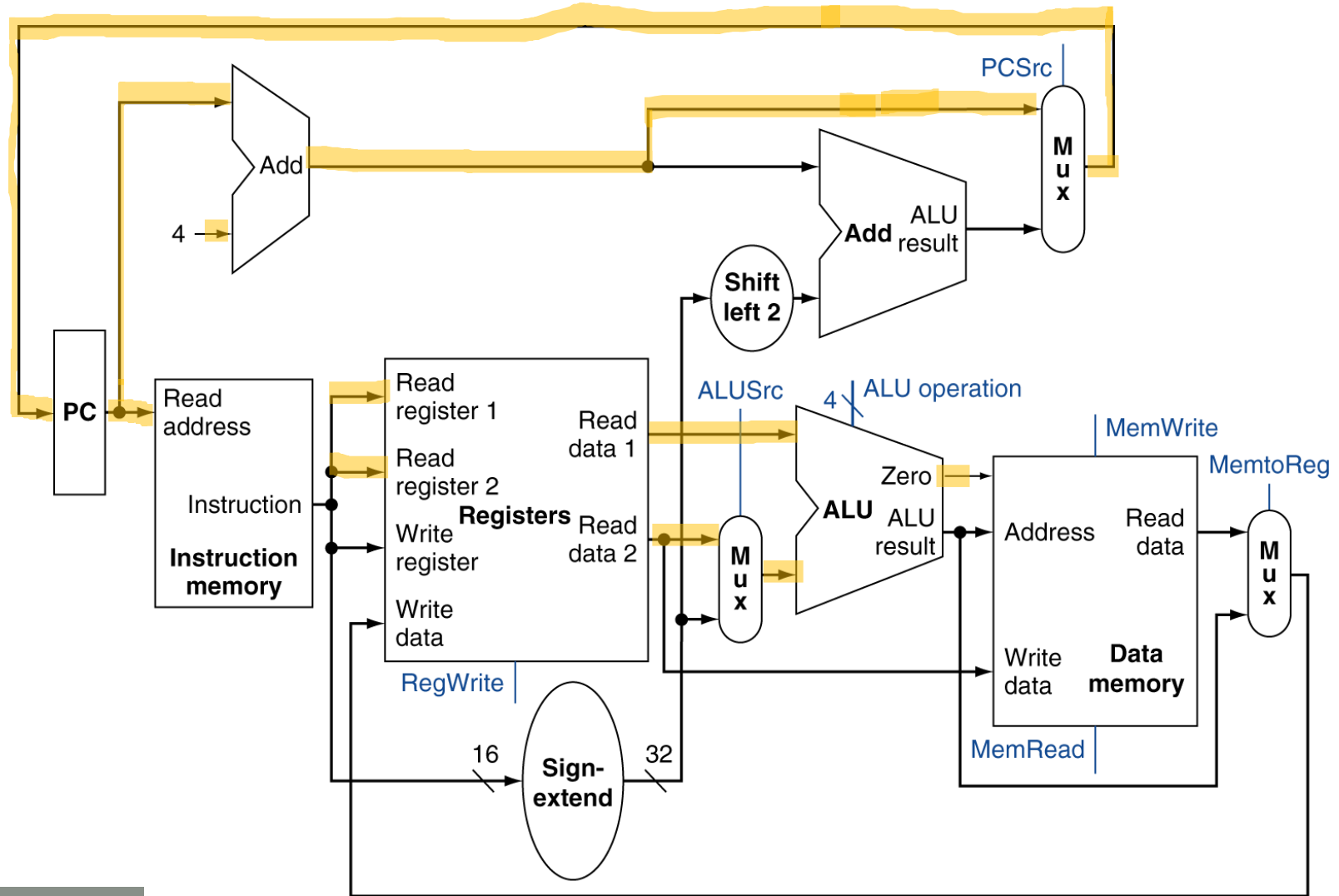

Instruction Execution Summary

Data path does an instruction in one clock cycle

1. Fetch: PC \rightarrow instruction memory \rightarrow instruction
2. Decode: Register numbers \rightarrow register file \rightarrow read registers
3. Execute: Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC \leftarrow target address or PC + 4

Problems to Solve

4.1, 4.7