

COMPUTER ARCHITECTURE
LAB4
PACKAGE AND COMPONENT

FCIS Ainshams University
Spring2021

AGENDA

- Component Mapping Example (hands-on):
Micro-operations: register load/ reset
- Package and Components
- Assignment: MIPS Package

COMPONENT MAPPING EXAMPLE

Using “FLOP REGISTER” module, implement the following micro-operations

C: R1 ← 0

L: R2 ← R1



How to solve this problem?

DESIGN STEPS...

To design any H/W module:

1. Define the components that will perform the required functionality
 - Ex: Mux's, Dec's, Reg's...etc.
2. Connect them together
3. Define suitable control signals to perform the required functionality
 - Ex: selections of Mux's, Loads of Reg's...etc.

Converting the draw to VHDL code becomes a **one-to-one mapping**

SOLUTION

C: $R1 \leftarrow 0$

L: $R2 \leftarrow R1$

1. Required components:

- 2 registers


2. Connections:

- R1 output connected to R2 input ($R2 \leftarrow R1$)

3. Control signals:


- When $C = 1$: $RST_{R1} = '1' \rightarrow RST_{R1} = C$
- When $L = 1$: $RST_{R2} = '0' \rightarrow RST_{R2} = \text{not}(L)$

FLOP REGISTER

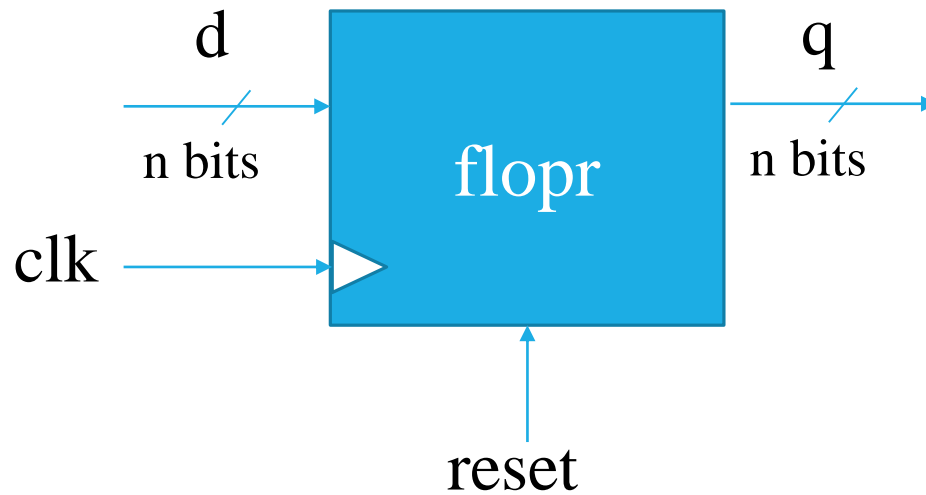

SOLUTION

 Then, the circuit that implements those micro-operations will look like the below



WAIT

- How can we use the previous implementation of the FLOP REGISTER?!
- We need some kind of reusability for our previous codes
- We need some kind of modularity for our previous codes (registers multiplexers decoders ...etc)
- Does VHDL support these needs ?

COMPONENT


- Declaring a code as a COMPONENT, provides a way of code partitioning and reusability.
- A COMPONENT is simply a piece of conventional code that contains (LIBRARY declarations, ENTITY and ARCHITECTURE)

DECLARING COMPONENT

- We can declare the component every time we use it.
- Or, we declare it once in a package and declare (include) this package in our code


DECLARING COMPONENT

Declare them in the main code itself

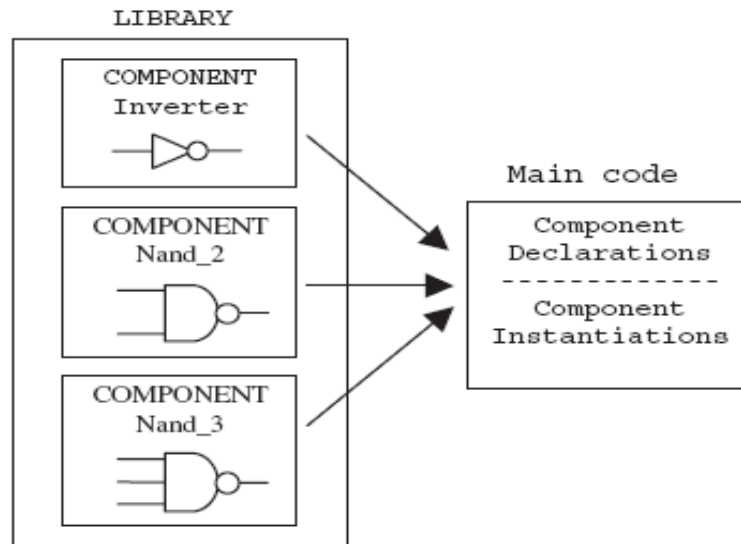

DECLARING COMPONENT

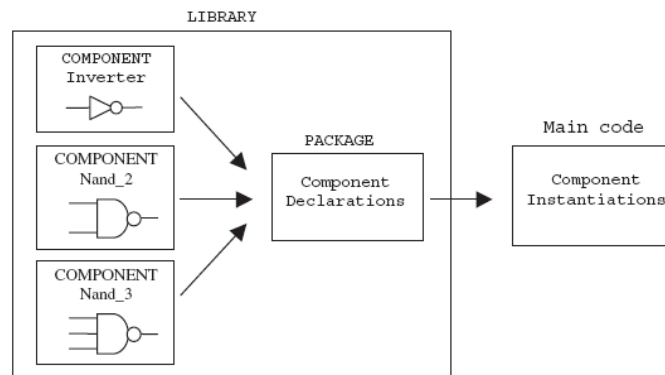- Otherwise, declare them in a PACKAGE
- This avoids repetition of its declaration every time the COMPONENT is instantiated.



FLOP REGISTER (AS AN ENTITY)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity flopr is
    generic (n : NATURAL := 32);
    port (clk, reset: in STD_LOGIC;
          d: in STD_LOGIC_VECTOR(n-1 downto 0);
          q: out STD_LOGIC_VECTOR(n-1 downto 0));
end Flopr;
architecture Behavioral of Flopr is
begin
    process (clk, reset)
    begin
        if reset='1' then q <= (others => '0');
        Elself rising_edge(clk) then
            q <= d;
        end if;
    end process;
end Behavioral;
```

FLOP REGISTER (AS A COMPONENT)

--MyPackage.vhd file

--Define flopr Component (**TYPICAL** as flopr Entity)

PACKAGE MyPackage **is**
Component flopr **is**

generic (n : **NATURAL** := 32);

port(clk, reset: **in** **STD_LOGIC**;

d: **in** **STD_LOGIC_VECTOR**(n-1 **downto** 0);

q: **out** **STD_LOGIC_VECTOR**(n-1 **downto** 0));


end Component;

end Behavioral;

MAIN MODULE (USES REGISTER)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use work.MyPackage.all;
```
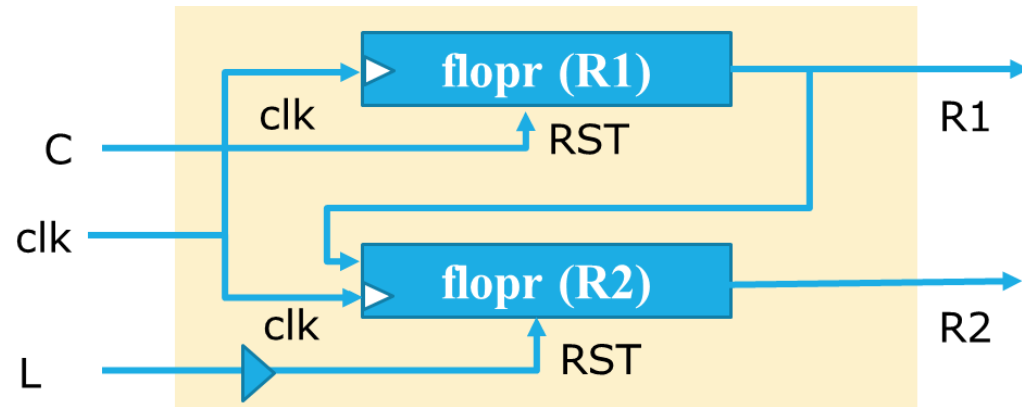
```
entity FloprMainModule is  
  generic (n : NATURAL := 32);  
  Port ( Clk : in STD_LOGIC;  
        C : in STD_LOGIC;  
        L : in STD_LOGIC;  
        R1 : out STD_LOGIC_VECTOR (n-1 downto 0);  
        R2 : out STD_LOGIC_VECTOR (n-1 downto 0));  
end FloprMainModule;
```




```
architecture Behavioral of FloprMainModule is  
  SIGNAL Tmp1: STD_LOGIC_VECTOR (n-1 DOWNTO 0);  
  SIGNAL Tmp2: STD_LOGIC_VECTOR (n-1 DOWNTO 0);  
  Begin  
    Tmp1 <= (others => '1');  
    R1Map: flopr GENERIC MAP (n) PORT MAP (clk,C,Tmp1,Tmp2);  
    R2Map: flopr GENERIC MAP (n) PORT MAP (clk,not(L),Tmp2,R2);  
    R1<= Tmp2 ;  
end Behavioral;
```

VHDL STEPS


To implement this example in Xilinx, you need to:

- Add the VHDL file of Register (flopr) to the project
- Add a package file to declare a component for it (MyPackage.vhd)
- Write the MainModule that describes the circuit using register component (MainModule.vhd)


ADDING A PACKAGE

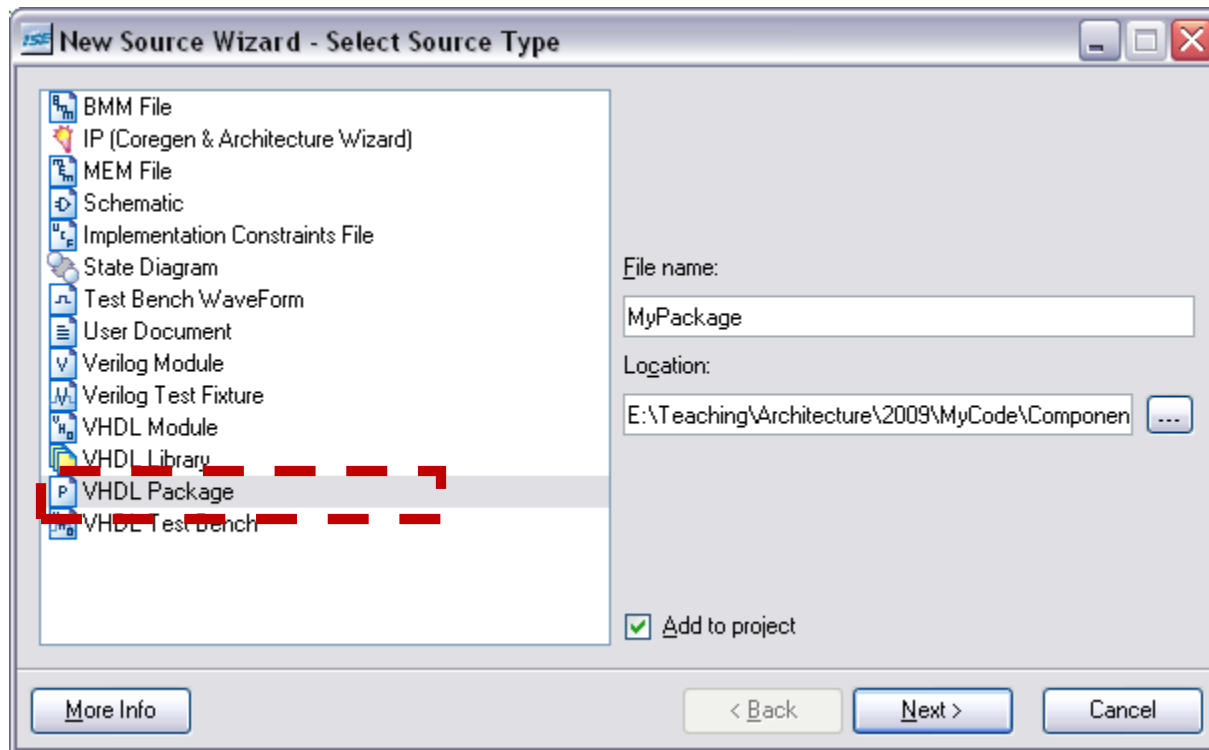

FINAL PROJECT CONTENT

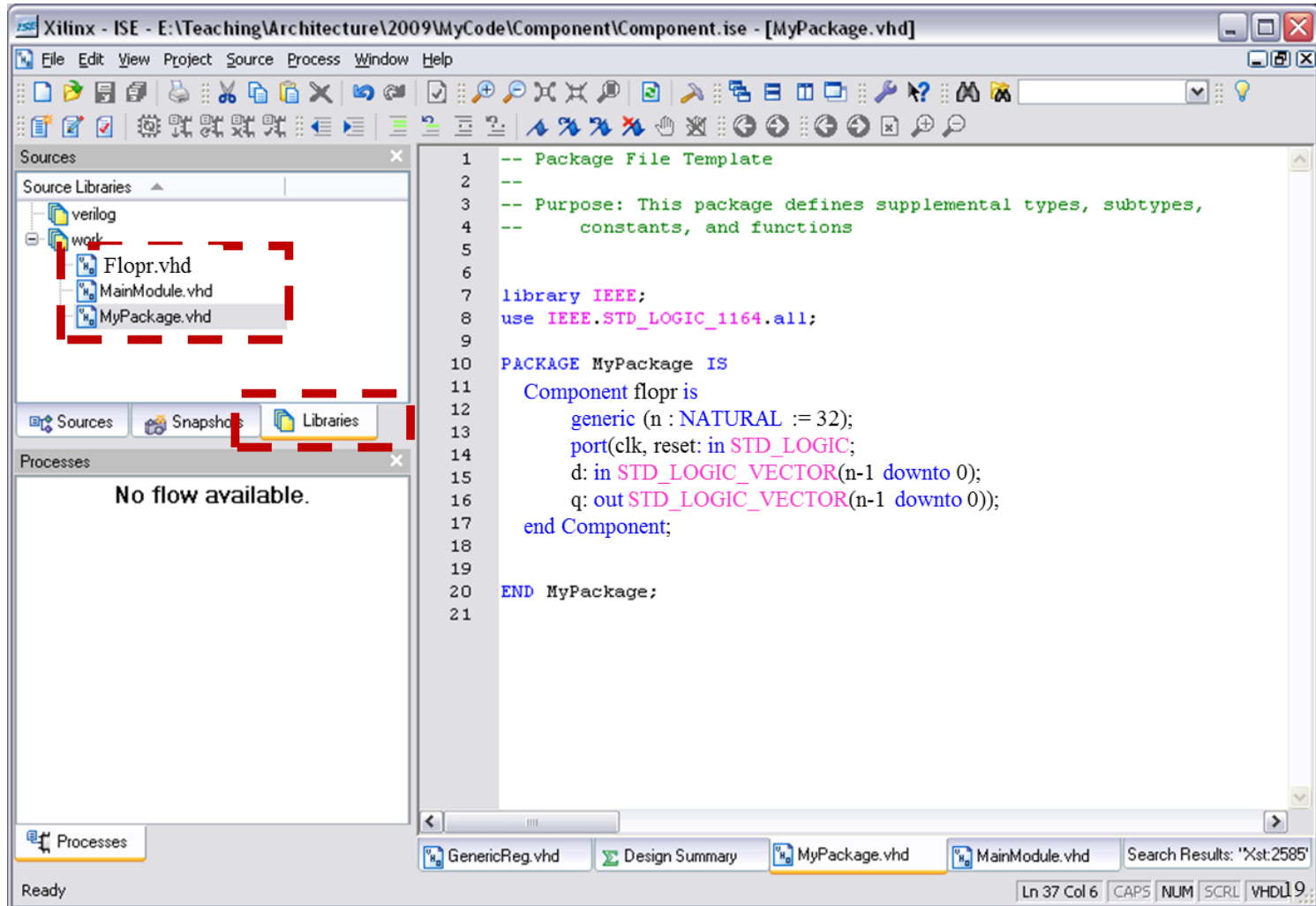

RTL DESIGN OF MAIN MODULE

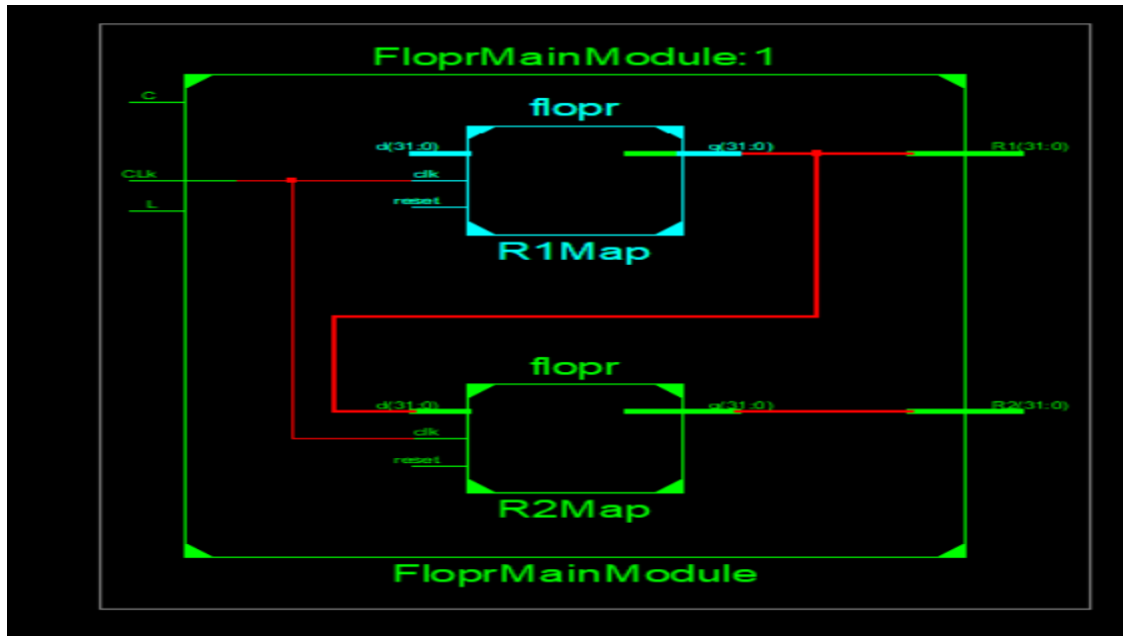

TEST BENCH

```
wait for clk_period/2 - 100ns;
```

```
l <= '1';
```

```
wait for clk_period;
```

```
c <= '1';
```

```
wait for clk_period*3;
```

```
c <= '0';
```

```
l <= '1';
```

```
wait;
```

ASSIGNMENT: MIPS PACKAGE

- Update “MyPackage” to be used while building the MIPS processor:

Create a component for each module implemented so far:

- flopr (already added)
- mux2
- S12
- Signext
- Alu
- Adder

ASSIGNMENT: MIPS PACKAGE

```
component flopr generic(n: integer);  
    port(clk, reset: in STD_LOGIC;  
        d: in STD_LOGIC_VECTOR(n-1 downto 0);  
        q: out STD_LOGIC_VECTOR(n-1 downto 0));  
end component;  
  
component mux2 generic(n: integer);  
    port(d0, d1: in STD_LOGIC_VECTOR(n-1 downto 0);  
        s: in STD_LOGIC;  
        y: out STD_LOGIC_VECTOR(n-1 downto 0));  
end component;  
  
component sl2  
    port(a: in STD_LOGIC_VECTOR(31 downto 0);  
        y: out STD_LOGIC_VECTOR(31 downto 0));  
end component;
```

ASSIGNMENT: MIPS PACKAGE

component signext

port(a: in `STD_LOGIC_VECTOR`(15 downto 0);

 y: out `STD_LOGIC_VECTOR`(31 downto 0));

end component;

component adder

port(a, b: in `STD_LOGIC_VECTOR`(31 downto 0);

 y: out `STD_LOGIC_VECTOR`(31 downto 0));

end component;

component alu

port(a, b: in `STD_LOGIC_VECTOR`(31 downto 0);

 alucontrol: in `STD_LOGIC_VECTOR`(2 downto 0);

 result: buffer `STD_LOGIC_VECTOR`(31 downto 0);

 zero: out `STD_LOGIC`);

end component;

UPCOMING LABS

- You must bring your package file in addition to the all .vhd files that have been implemented so far:
 - Adder
 - S12
 - Signext
 - flopr
 - mux2
 - Alu



Thanks